


08/29/17

LECTURE 1

- READING: Chapters 1 & 2 of SG&O
- THE CENTRAL PROBLEM IN POWER SYSTEMS
- REVIEW OF PHASORS
- POWER: INSTANTANEOUS, AVERAGE & COMPLEX

THE CENTRAL PROBLEM IN POWER SYSTEMS

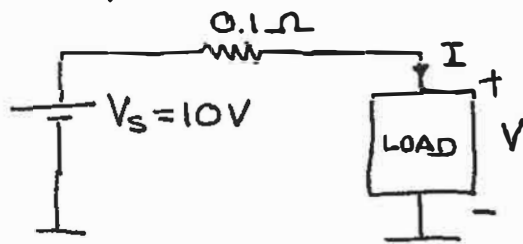- It is to compute all electric variables given load consumptions. In a nutshell with a simple DC system



LOAD
 $P = 10W$, What are the values of V & I ?

Power:

$$\left. \begin{array}{l} V \cdot I = P = 10 \\ V_s = 0.1 \cdot I + V \end{array} \right\} \rightarrow I = \frac{10 - V}{0.1} \left\{ \begin{array}{l} \rightarrow 10 = V \cdot \left(\frac{10 - V}{0.1} \right) \rightarrow \\ 10 = V \cdot I \end{array} \right.$$

$$\rightarrow 1 = 10V - V^2 = 0 \rightarrow V^2 - 10V + 1 = 0$$

$$V = \frac{10 \pm \sqrt{10^2 - 4}}{2} = \begin{cases} \frac{10 + \sqrt{96}}{2} = 9.8990V \rightarrow I = 1.01A \\ \frac{10 - \sqrt{96}}{2} = 0.1010V \rightarrow I = 98.99A \end{cases}$$

Both solutions are possible in real life.


- The first one represents a case when the system is working properly (good voltage on the load, small currents)

- The second case is typical of a situation where there could be a fault (a short-circuit). We are interested in understanding this case to size properly conductors and to set protections properly.


REVIEW OF PHASORS

- The systems we will study extensively in this class are AC electric power systems.
- The use of phasors is very convenient to ~~solve~~ formulate and solve problems of interest.

- Let's go back to the DC example.

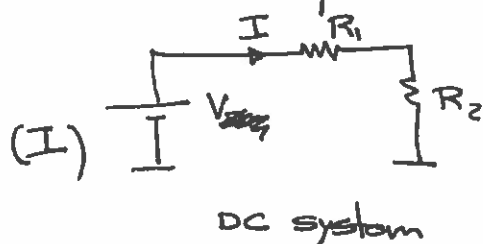

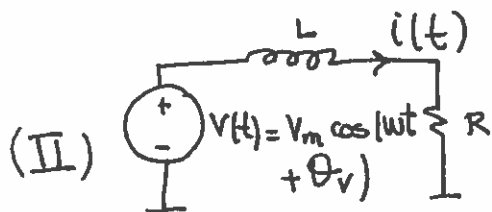$V_{R_2} = (R_1 + R_2) I \rightarrow$ this is an algebraic expression, which we know how to manipulate.




Kirchoff's laws always apply, i.e., the physics holds, so we can write the following diff eq:


$$v(t) = R \cdot i(t) + L \cdot \frac{di}{dt}$$

Q: Can we use some trick to represent (II) in such a way that we can use algebraic representation instead of differential equation? Hopefully, this will make our lives easier

A: YES! PHASORS!!

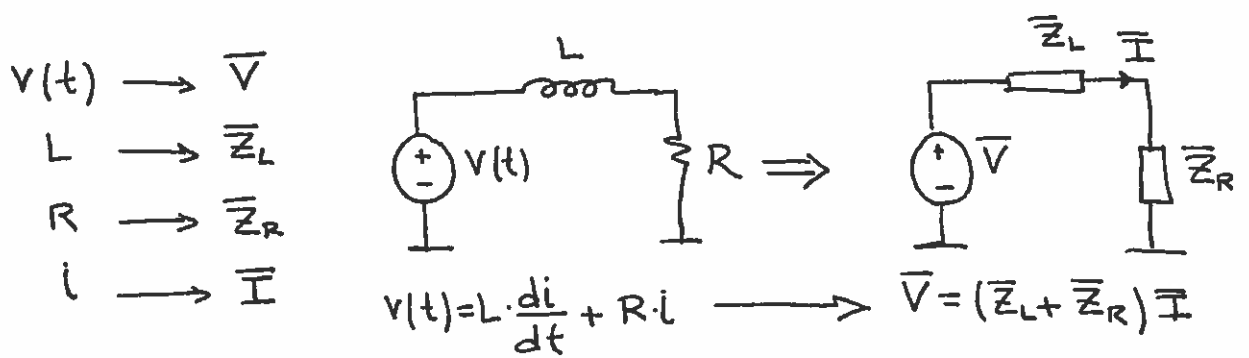

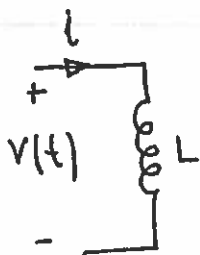Q: How do we go from $v(t), L, R$ to $\bar{V}, \bar{Z}_L, \bar{Z}_R$?



$$v(t) = L \cdot \frac{di}{dt}$$

$$v(t) = V_m \cos(\omega t + \theta_v) = L \cdot \frac{di}{dt}$$

In steady-state: $i(t) = I_m \cdot \cos(\omega t + \theta_i)$

$$V_m \cos(\omega t + \theta_v) = -L \cdot I_m \omega \sin(\omega t + \theta_i)$$

But $-\sin(\omega t + \theta_i) = \cos(\theta_i + \frac{\pi}{2} + \omega t)$

$$V_m \cos(\omega t + \theta_v) = L \cdot I_m \omega \cdot \cos(\omega t + \theta_i + \frac{\pi}{2})$$

$$I_m = \frac{V_m}{\omega L} \quad \theta_i = \theta_v - \frac{\pi}{2}$$

Now let's add and subtract $j V_m \sin(\omega t + \theta_v)$ and $j L I_m \omega \cos(\omega t + \theta_i + \frac{\pi}{2})$:

$$V_m \cdot \cos(\omega t + \theta_v) + j \sin(\omega t + \theta_v) = L \cdot I_m \cdot \omega \cos(\omega t + \theta_i + \frac{\pi}{2}) + j I_m \omega \sin(\omega t + \theta_i + \frac{\pi}{2})$$

Euler's expansion:

$$e^{j\theta} = \cos \theta + j \sin \theta$$

Then:

$$V_m e^{j(\theta_v + \omega t)} = L \cdot \omega I_m e^{j(\theta_i + \omega t + \pi/2)}$$

$$V_m e^{j\theta_v} \cdot e^{j\omega t} = L \omega I_m e^{j(\theta_i + \pi/2)} e^{j\omega t} = L \cdot \omega I_m e^{j\pi/2} \cdot e^{j\theta_i} = L \omega \cdot e^{j\pi/2} I_m e^{j\theta_i}$$

Let's define: $\bar{V} \triangleq \frac{V_m}{\sqrt{2}} e^{j\theta_v} = L \omega \cdot e^{j\pi/2} I_m e^{j\theta_i}$

$$\bar{I}_m \triangleq \frac{I_m}{\sqrt{2}} e^{j\theta_i}$$

$$\bar{Z}_L \triangleq j\omega L$$


So we get: $\bar{V} = \bar{Z}_L \cdot \bar{I}$!

Similarly, we can get:

$$C \rightarrow \frac{1}{j\omega C}$$

$$R \rightarrow R$$

INSTANTANEOUS POWER

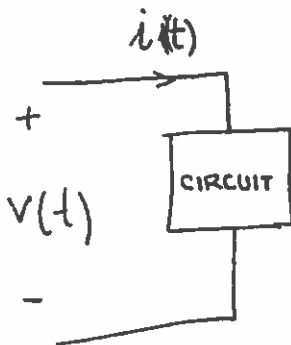

$$P(t) = V(t) \cdot i(t)$$

$$V(t) = V_m \cos(\omega t + \theta_v)$$

$$i(t) = I_m \cos(\omega t + \theta_i)$$

$$P(t) = V_m I_m \cos(\omega t + \theta_v) \cos(\omega t + \theta_i)$$

ROOT-MEAN SQUARE

$$V_{\text{RMS}} = \sqrt{\frac{1}{T} \int_0^T v^2(t) dt} = \frac{V_m}{\sqrt{2}}$$

Instead of $\bar{V} = \frac{V_m}{\sqrt{2}} < \theta_v$, we can define \bar{V} as: $\bar{V} = V_{\text{RMS}} < \theta_v$.

Average power then becomes:

$$P = V_{\text{RMS}} \cdot I_{\text{RMS}} \cdot \cos(\theta_v - \theta_i)$$

From now onwards, we drop RMS and just use V to represent the RMS value of $v(t) = V_m \cos(\omega t + \theta_v)$

COMPLEX POWER

Let's do a similar calculation, but instead of using $v(t)$ and $i(t)$, let's use \bar{V} and \bar{I}

$$\bar{S} \triangleq \bar{V} \bar{I}^* = V e^{j\theta_v} \cdot I e^{-j\theta_i} = V \cdot I e^{j(\theta_v - \theta_i)}$$

$$\bar{S} = \underbrace{VI}_{P} \left[\cos(\theta_v - \theta_i) + j \sin(\theta_v - \theta_i) \right]$$

$$\boxed{Q \triangleq VI \sin(\theta_v - \theta_i)}$$

← Reactive power →


→ doesn't do anything for us but it is extremely important for maintaining voltage.

Reminder: $\cos(\theta_1) \cdot \cos(\theta_2) = \frac{1}{2} [\cos(\theta_1 - \theta_2) + \cos(\theta_1 + \theta_2)]$

Thus:

$$P(t) = \frac{1}{2} V_m I_m \cdot [\cos(\theta_v - \theta_i) + \cos(2\omega t + \theta_v + \theta_i)]$$
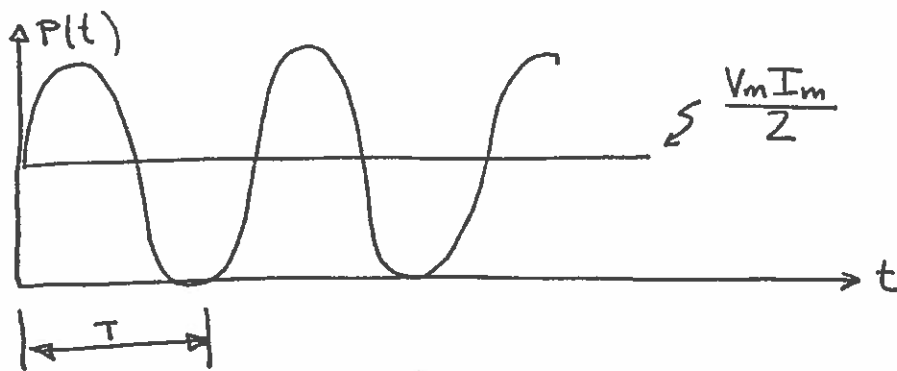
$$P(t) = \frac{V_m I_m}{2} \cos(\theta_v - \theta_i) + \frac{V_m I_m}{2} \cos(2\omega t + \theta_v + \theta_i)$$



AVERAGE POWER

$$P = \frac{1}{T} \int_0^T \frac{VI}{2} [\cos(\theta_v - \theta_i) + \cos(2\omega t + \theta_v + \theta_i)] dt =$$

$$= \frac{V_m I_m}{2} \cos(\theta_v - \theta_i) + \frac{1}{T} \int_0^T \cos(2\omega t + \theta_v + \theta_i) dt =$$

$$= \frac{V_m I_m}{2} \cos(\theta_v - \theta_i) + \frac{1}{2\omega T} \sin(2\omega t + \theta_v + \theta_i) \Big|_0^T$$

$$P = \frac{V_m I_m}{2} \cos(\theta_v - \theta_i)$$

POWER FACTOR

$$PF \triangleq \cos(\theta_v - \theta_i)$$