


09/05/17

LECTURE 3

- POWER IN THREE-PHASE SYSTEMS
- ANALYSIS OF Y-Δ CONNECTIONS
- OTHER TYPES OF CONNECTIONS
- PER-PHASE EQUIVALENTS (Y-Δ TRANSFORMATION)
- EXAMPLES

POWER IN 3φ SYSTEMS

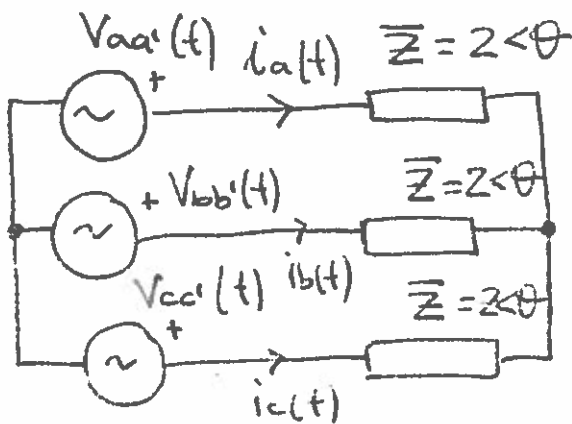We saw that in balanced three-phase systems, all triplets form a balanced three-phase system.



$$V_{aa'}(t) = \sqrt{2} V \cos(\omega t)$$

$$V_{bb'}(t) = \sqrt{2} V \cos(\omega t - \frac{2\pi}{3})$$

$$V_{cc'}(t) = \sqrt{2} V \cos(\omega t + \frac{2\pi}{3})$$

$$i_a(t) = \sqrt{2} I \cos(\omega t - \theta)$$

$$i_b(t) = \sqrt{2} I \cos(\omega t - \frac{2\pi}{3} - \theta)$$

$$i_c(t) = \sqrt{2} I \cos(\omega t + \frac{2\pi}{3} - \theta)$$

$$P_a(t) = VI [\cos(\theta) + \cos(2\omega t - \theta)]$$

$$P_b(t) = VI [\cos(\theta) + \cos(2\omega t - \theta - \frac{4\pi}{3})]$$

$$P_c(t) = VI [\cos(\theta) + \cos(2\omega t - \theta + \frac{4\pi}{3})]$$

$$P_{3\phi}(t) = P_a(t) + P_b(t) + P_c(t) \\ = 3VI \cos(\theta) + 0$$

$$P_{3\phi}(t) = 3VI \cos(\theta) = P \quad \leftarrow \text{instantaneous power is constant}$$

~~AC POWER~~

Recall that here V and I are phase voltage and current ($V \equiv V_{\phi}$, $I \equiv I_{\phi}$)

$$V_L \equiv \sqrt{3} V_{\phi}, \quad I_L = I_{\phi}$$

$$P_{3\phi} = \sqrt{3} V_L \cdot I_L \cdot \cos(\theta) \quad \leftarrow \text{This formula is universal and work for any connection (Y-Δ)}$$

COMPLEX POWER


$$\vec{S}_{3\phi} = \vec{S}_a + \vec{S}_b + \vec{S}_c$$

$$= 3VI \cdot [\cos \theta + j \sin \theta]$$



$$= \sqrt{3} V_L \cdot I_L \cdot [\cos \theta + j \sin \theta]$$

$$\left. \begin{aligned} P &= \sqrt{3} V_L \cdot I_L \cdot \cos(\theta) \\ Q &= \sqrt{3} V_L \cdot I_L \cdot \sin(\theta) \end{aligned} \right\} \text{Universal formulas.}$$

ANALYSIS OF Y-Δ CONNECTION

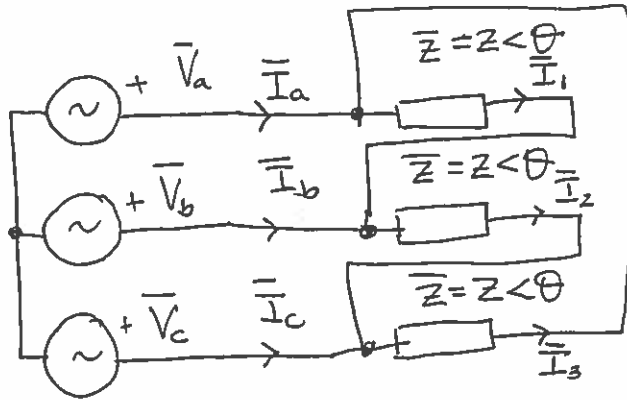
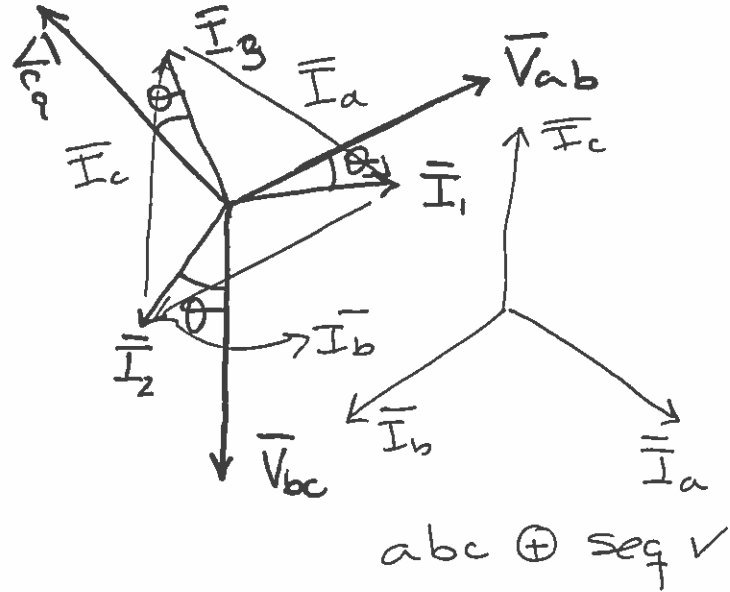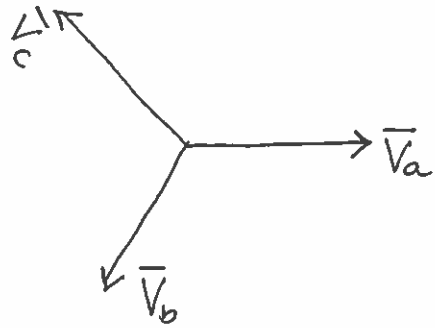
$$\theta \leq \theta \leq \frac{\pi}{2}$$



$$\begin{aligned} \bar{I}_a &= \bar{I}_1 - \bar{I}_3 \\ \bar{I}_b &= \bar{I}_2 - \bar{I}_1 \\ \bar{I}_c &= \bar{I}_3 - \bar{I}_2 \end{aligned}$$

3 ϕ power (Δ)


$$\begin{aligned} P_{3\phi} &= 3 \cdot V_{ab} \cdot I_1 \cos \theta \\ &= 3 V_{ab} \cdot \frac{I_a}{\sqrt{3}} \cos \theta \\ Q_{3\phi} &= 3 V_{ab} I_1 \sin \theta \\ &= 3 V_{ab} \cdot \frac{I_a}{\sqrt{3}} \sin \theta \end{aligned}$$

$$\begin{aligned} V_{ab} &\equiv I_L \\ I_1 &= \frac{I_a}{\sqrt{3}} = \frac{I_L}{\sqrt{3}} \end{aligned}$$


$$\begin{aligned} P_{3\phi} &= \sqrt{3} V_L \cdot I_L \cdot \cos \theta \\ Q_{3\phi} &= \sqrt{3} V_L \cdot I_L \sin \theta \end{aligned}$$

← Same as the Y connection.

OTHER TYPES OF CONNECTIONS

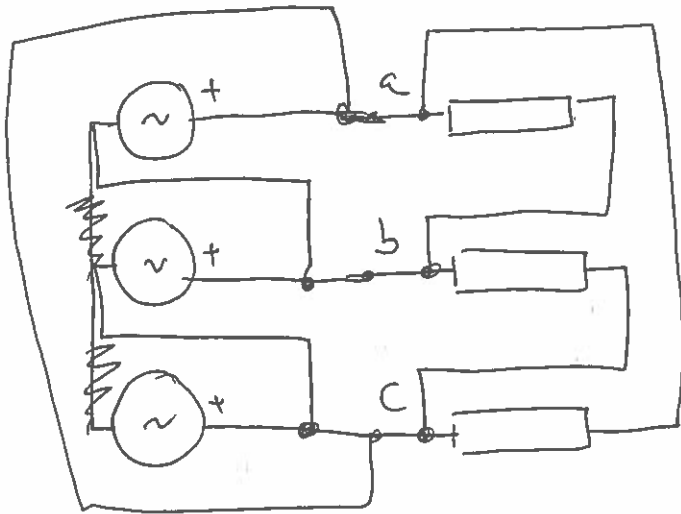


$\Delta-\Delta$ CONN.

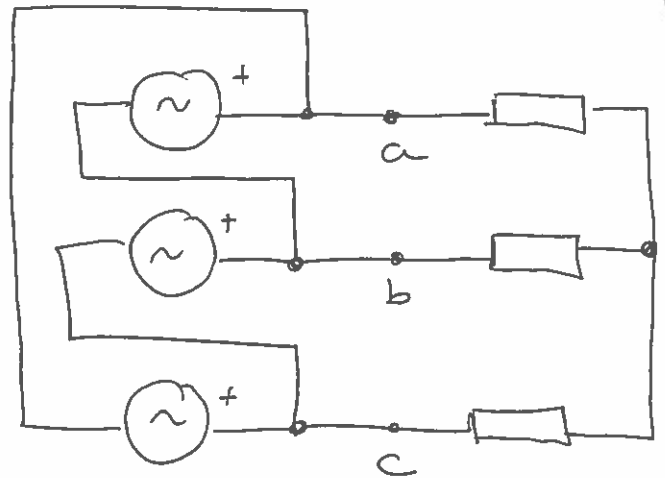


$\Delta-Y$ CONN.

PER-PHASE EQUIVALENTS

We have shown that

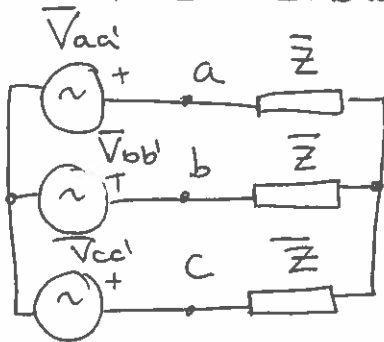


\equiv



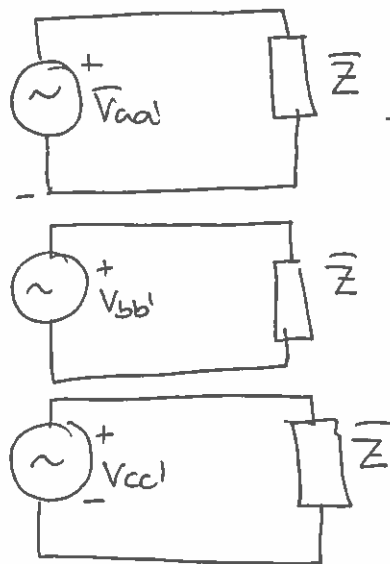


per-phase equivalent

What about ?

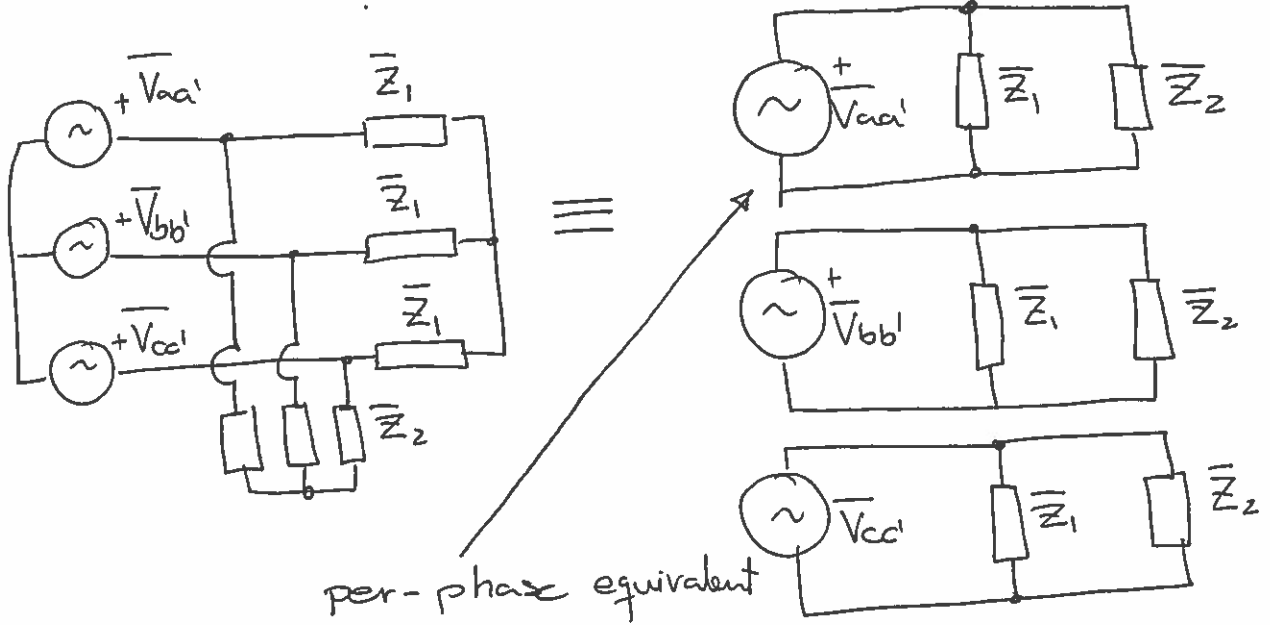


What about ?

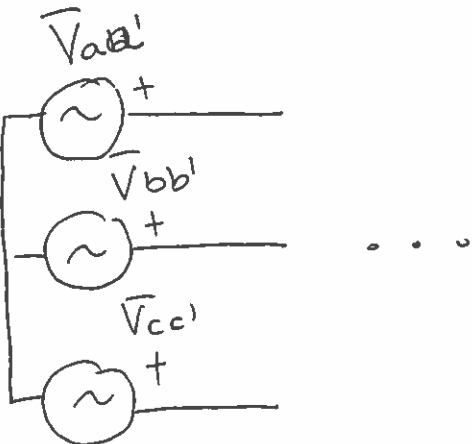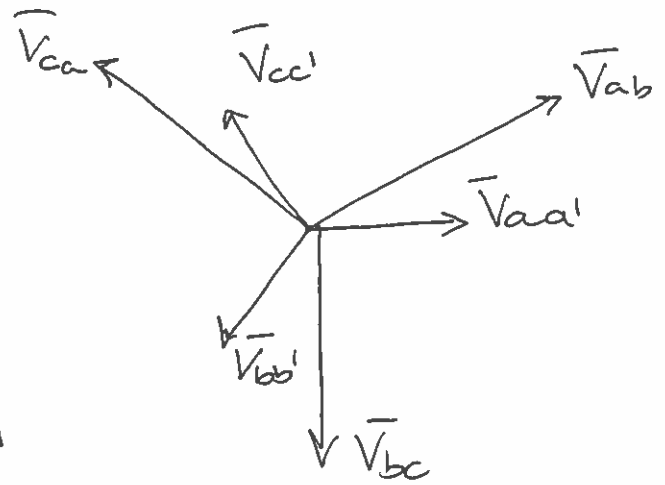
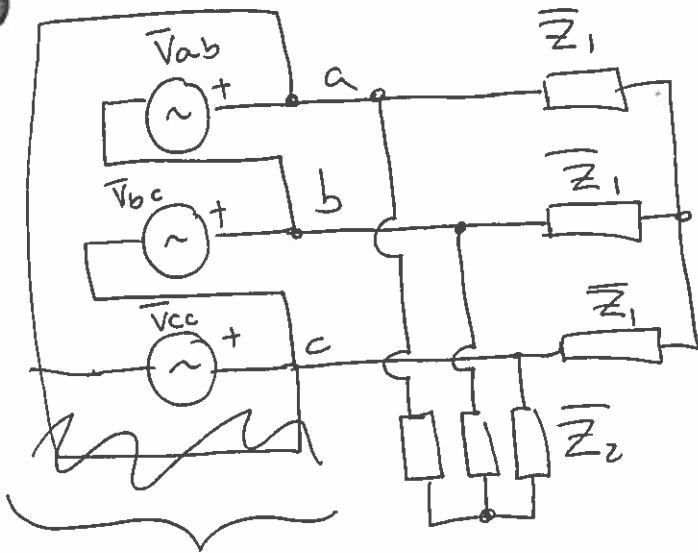


→ The rest is the same as above.

What about?

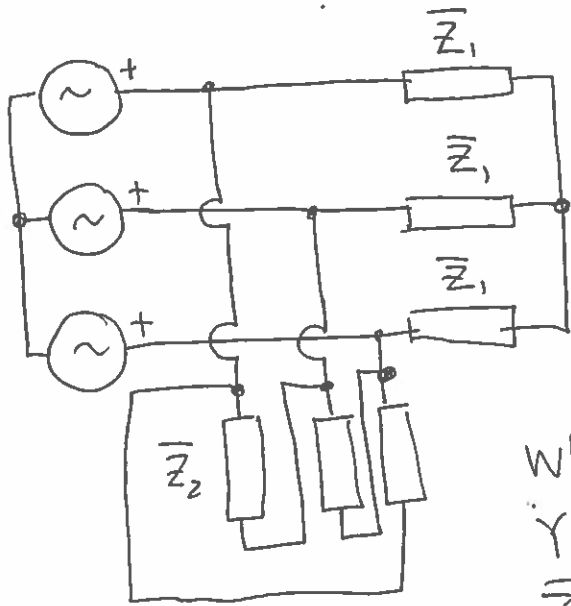

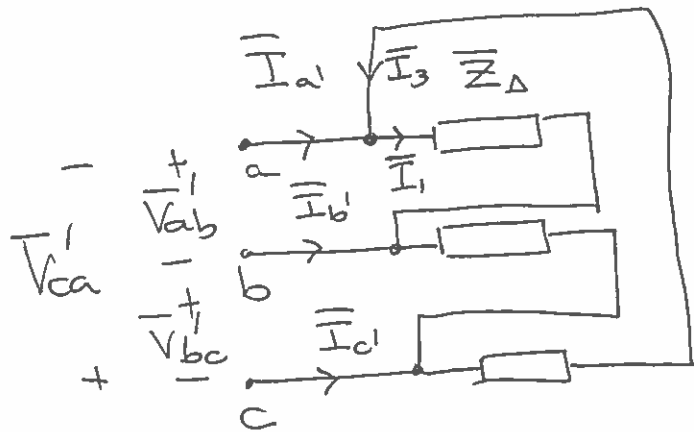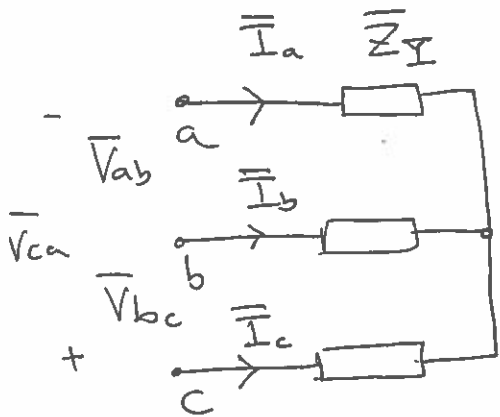What we somehow find a \bar{Y} -equivalent of the \bar{Z}_2 load? If so, we are back to case 1. [We sort of did that already for the Δ -connected voltage source.]



What is the relation between \bar{Z}_Y and \bar{Z}_Δ

so that

$$\bar{V}_{ab} = \bar{V}'_{ab}$$

$$\bar{V}_{bc} = \bar{V}'_{bc}$$

$$\bar{V}_{ca} = \bar{V}'_{ca}$$

\Rightarrow

$$\bar{I}_a = \bar{I}'_a$$

$$\bar{I}_b = \bar{I}'_b$$

$$\bar{I}_c = \bar{I}'_c$$

$$\bar{Z}_Y = \frac{1}{3} \bar{Z}_\Delta$$

Δ - connection

$$\bar{I}'_a = \bar{I}_1 - \bar{I}_3$$

$$= \frac{\bar{V}_{ab}}{\bar{Z}_\Delta} - \frac{\bar{V}_{ca}}{\bar{Z}_\Delta} = \frac{\bar{V}'_{ab} - \bar{V}'_{ca}}{\bar{Z}_\Delta}$$

Y connection

$$\bar{V}_{ab} = \bar{I}_a \cdot \bar{Z}_Y - \bar{I}_b \cdot \bar{Z}_Y$$

$$\bar{V}_{ca} = \bar{I}_c \cdot \bar{Z}_Y - \bar{I}_a \cdot \bar{Z}_Y$$

$$\frac{\bar{V}_{ab} - \bar{V}_{bc}}{\bar{Z}_Y} = \bar{I}_a + \bar{I}_b + \bar{I}_c = 3\bar{I}_a$$

$$\bar{V}_{ab} - \bar{V}_{bc} = 3\bar{Z}_Y \cdot \bar{I}_a$$

$$\bar{V}'_{ab} - \bar{V}'_{ca} = \bar{Z}_\Delta \cdot \bar{I}_a$$

$$\bar{Z}_\Delta = 3 \cdot \bar{Z}_Y$$

$$\bar{Z}_Y = \frac{1}{3} \bar{Z}_\Delta$$

PROBLEM

LOAD #1: Y -CONNECTED LOAD, 100KVA (3 ϕ), 0.9 PF lag

LOAD #2: Y -CONNECTED LOAD, 60KW (3 ϕ), 0.7 PF lead

LOAD #3: Δ -CONNECTED LOAD, 75A (phase current), 0.9 PF lag

a) Total complex power (3 ϕ)

$$\text{LOAD 1: } \bar{S}_1 = 100 \cdot (0.9 + j \sin(\cos^{-1}(0.9))) \\ = 90 + j43.6$$

$$\text{LOAD 2: } \bar{S}_2 = 60 - j61.21$$

LOAD 3:

$$I_\phi = 75 \text{ A} \quad S_3 = \sqrt{3} \cdot V_L \cdot I_L \\ I_L = \sqrt{3} \cdot 75 = 129.9 \text{ A} \quad = \sqrt{3} \cdot 480 \cdot 129.9 \\ = 108 \text{ KVA}$$

$$\bar{S}_3 = 108 (0.9 + j \sin(\cos^{-1}(0.9))) \\ = 97.2 + j47.06$$

$$\bar{S}_T = \bar{S}_1 + \bar{S}_2 + \bar{S}_3 = (90 + 60 + 97.2) \\ + j(43.6 - 61.21 + 47.06) \\ = 247.2 + j29.45$$

$$S_T = 248.94 \text{ KVA}$$

b)
$$I_L = \frac{S_T}{\sqrt{3} V_L} = \frac{248.94 \cdot 10^3}{\sqrt{3} \cdot 480} = 299.43 \text{ A} \\ \approx 300 \text{ A}$$

c)
$$Q_T = 29.45 \rightarrow \text{Need to add} \\ Q_c = -29.45 \rightarrow \\ Q_c/3 = -9.82 \text{ KVAR} \\ \text{to be added per phase}$$

d)
$$I'_L = \frac{S'_T}{\sqrt{3} V_L} = \frac{247.2 \cdot 10^3}{\sqrt{3} \cdot 480} = 297.33 \text{ A}$$