


LECTURE 8

09/21/17

NON-IDEAL TRANSFORMER MODEL

Assumptions:

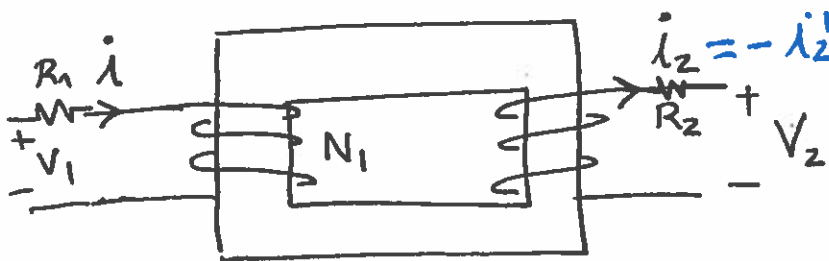- losses: $R_1 \neq 0, R_2 \neq 0$
- Flux leakage, $\Phi_{e1}, \Phi_{e2} \neq 0$
- Finite permeability, $\mu < \infty$.



$$V_1 = R_1 i_1 + \frac{d\lambda_1}{dt}$$

$$V_2 = -R_2 i_2 + \frac{d\lambda_2}{dt}$$

$$\lambda_1 = N_1 (\underbrace{\Phi_{11} + \Phi_{12}}_{\Phi_m} + \Phi_{e1}) = N_1 \Phi_m + \underbrace{\Phi_{e1} N_1}_{\lambda_{e1}}$$

$$\lambda_2 = N_2 (\underbrace{\Phi_{22} + \Phi_{21}}_{\Phi_m} + \Phi_{e2}) = N_2 \Phi_m + \underbrace{\Phi_{e2} N_2}_{\lambda_{e2}}$$

Assumption: (linearity of the magnetic circuit)

$$\lambda_{e1} = N_1 \Phi_{e1} = L_{e1} \cdot \dot{i}_1$$

$$\lambda_{e2} = N_2 \Phi_{e2} = L_{e2} \dot{i}_2 = -L_{e2} \cdot \dot{i}_2'$$

$$\begin{cases} V_1 = R_1 i_1 + L_{e1} \frac{di_1}{dt} + N_1 \frac{d\Phi_m}{dt} \\ V_2 = -R_2 i_2' - L_{e2} \frac{di_2'}{dt} + N_2 \frac{d\Phi_m}{dt} \end{cases}$$

$$V_1 = R_1 i_1 + L e_1 \frac{di_1}{dt} + \underbrace{N_1 \frac{d\phi_m}{dt}}_{e_1}$$

$$V_2 = -R_2 i_2 - L e_2 \frac{di_2}{dt} + \underbrace{N_2 \frac{d\phi_m}{dt}}_{e_2}$$

$$N_1 i_1 - N_2 i_2 = R \phi_m$$

with secondary open: $N_1 i_1 = R \phi_m \rightarrow i_m = \frac{R \phi_m}{N_1}$

$$i_1 = \frac{R}{N_1} \phi_m =: i_m$$

Assumption: (linearity of the magnetic circuit)

$$\lambda_m = N_1 \phi_m = L_m i_m$$

$$e_1 = \frac{d\lambda_m}{dt} = L_m \frac{di_m}{dt}$$


• $V_1 = R_1 i_1 + L e_1 \frac{di_1}{dt} + e_1 \checkmark$

• $V_2 = -R_2 i_2 - L e_2 \frac{di_2}{dt} + e_2 \checkmark$


• $\frac{e_1}{e_2} = \frac{N_1}{N_2} \checkmark$

• $e_1 = L_m \frac{di_m}{dt} \checkmark$

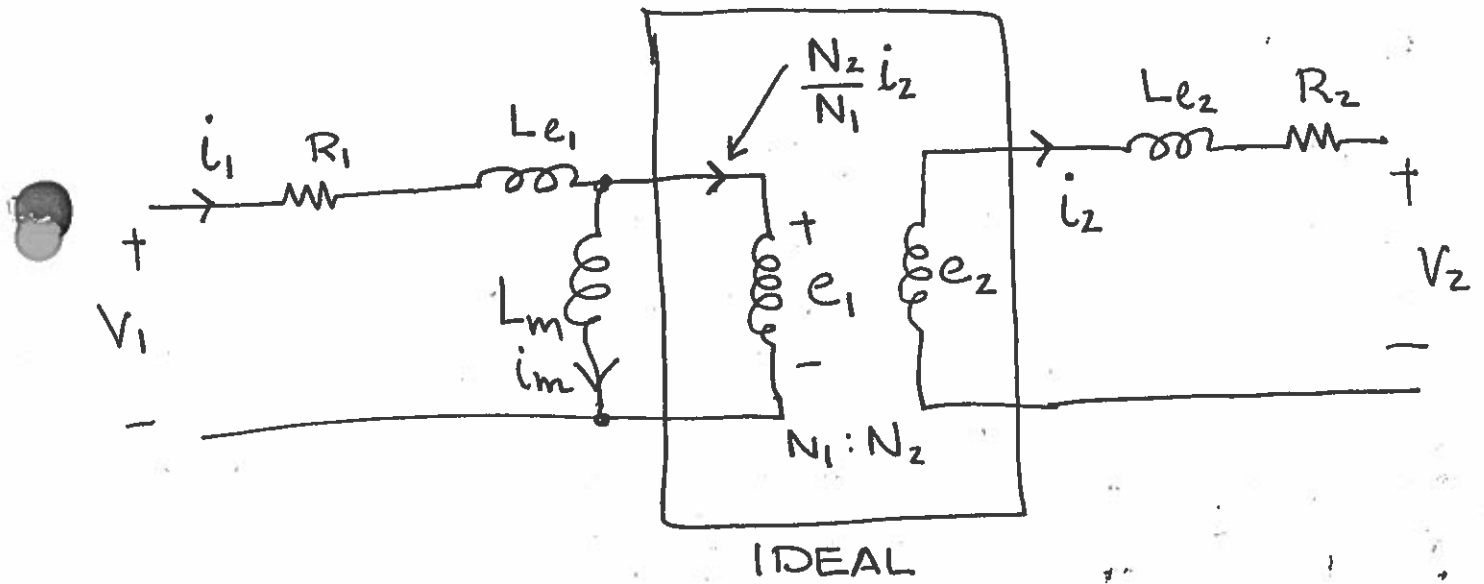
• $i_1 = \frac{N_2}{N_1} i_2 + i_m \checkmark$



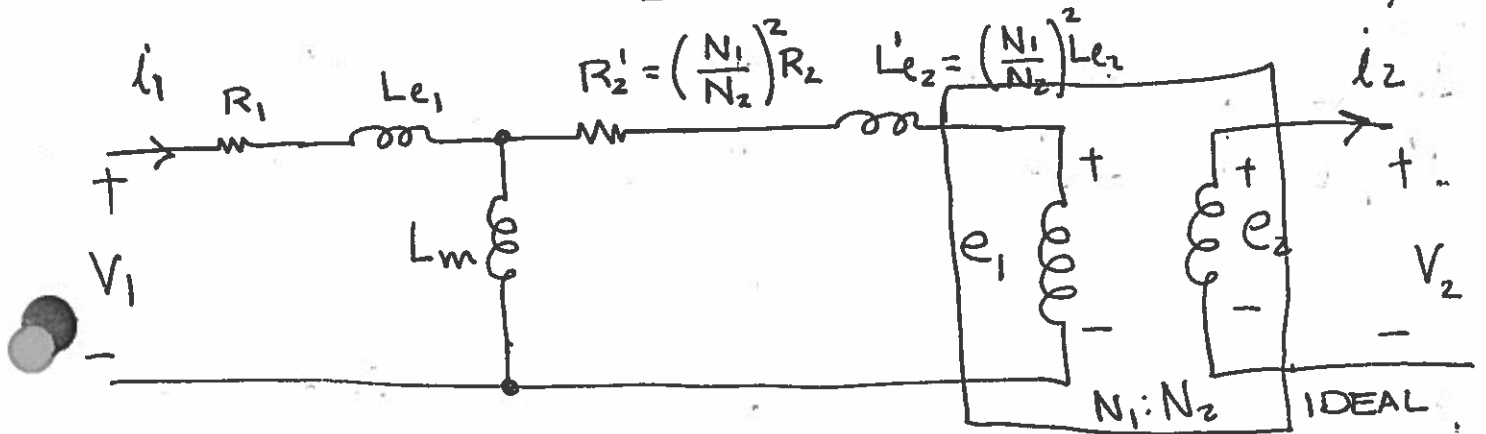We can refer L_{e2} and R_2 to the primary



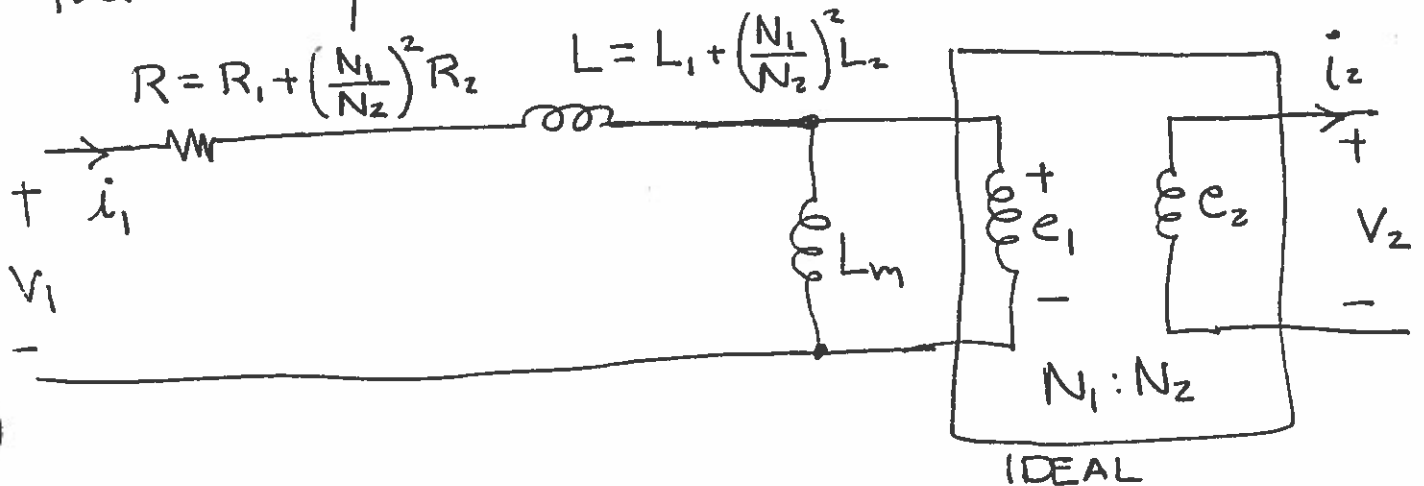
L_m is very large, whereas R'_2 and L'_{e2} are very small in comparison, thus we can swap them to get:




SEE (2b)

THREE-PHASE TRANSFORMERS

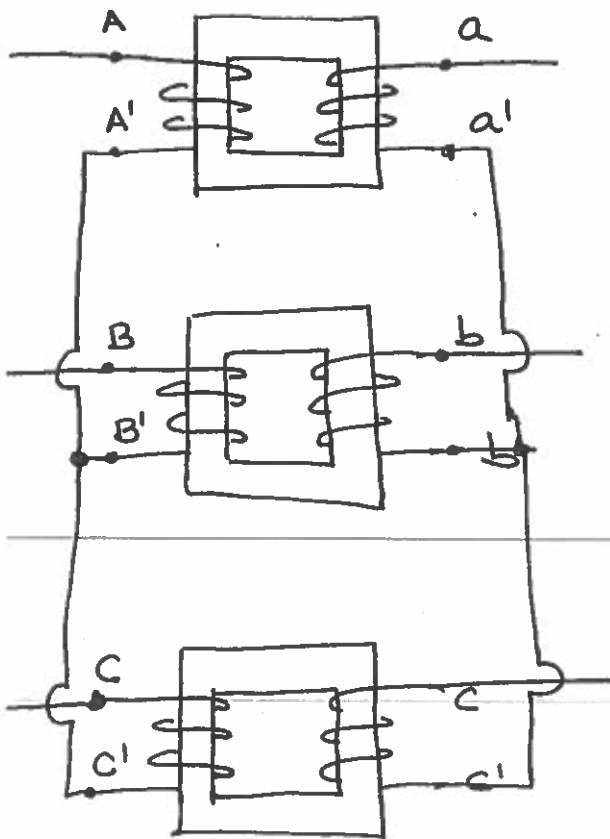We can construct a 3ϕ transformer by interconnecting three 1ϕ transformers




Y-Y CONNECTION

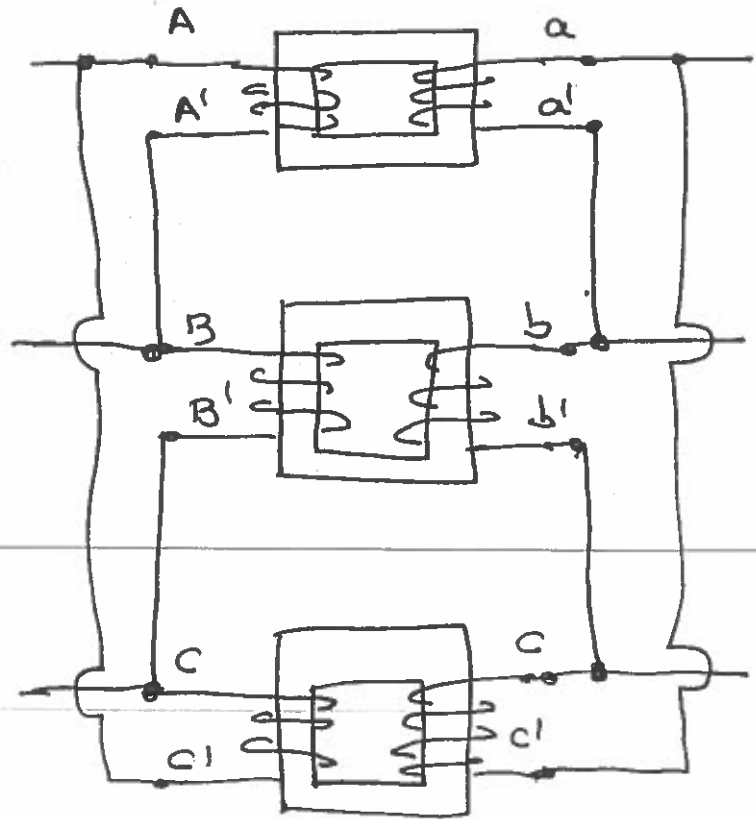

Δ - Δ CONNECTION


- The type of connection, i.e., Y-Y, Δ - Δ , Δ -Y, or Y- Δ depends on the application e.g., a step-up transformer for connecting a generator to the grid vs a step-down transformer used in distribution.

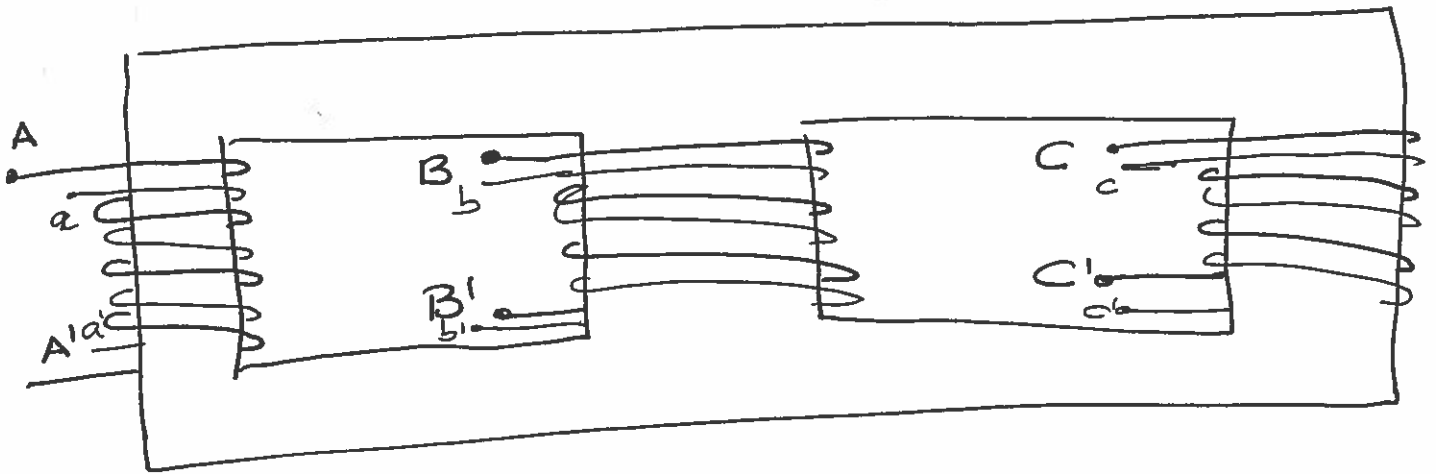- It is very common (specially for small- and medium-size) transformers to use a single core



Y-Y TRANSFORMER

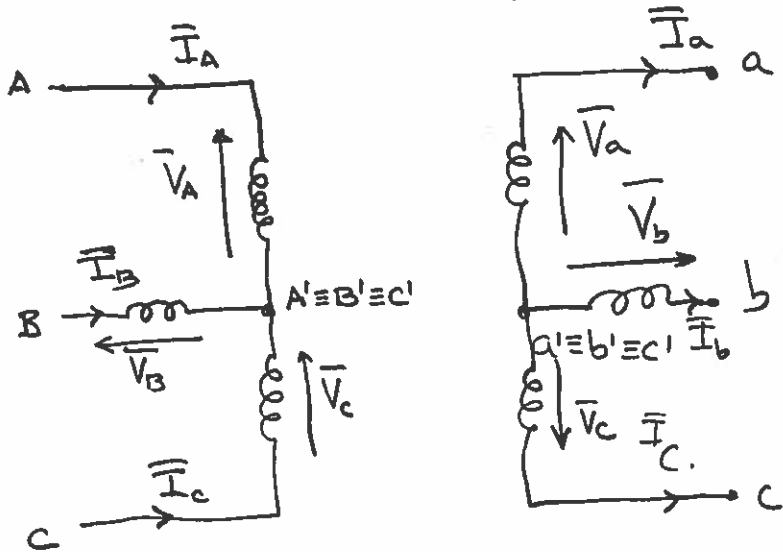
- Turn ratio of individual transformers is a
- No phase-shifting
- Possibility of grounding both sides of the transformer



$$\frac{\bar{V}_A}{\bar{V}_a} = \frac{\bar{V}_B}{\bar{V}_b} = \frac{\bar{V}_C}{\bar{V}_c} = a$$



$$\frac{\bar{I}_A}{\bar{I}_a} = \frac{\bar{I}_B}{\bar{I}_b} = \frac{\bar{I}_C}{\bar{I}_c} = \frac{1}{a}$$

Per-phase equivalent

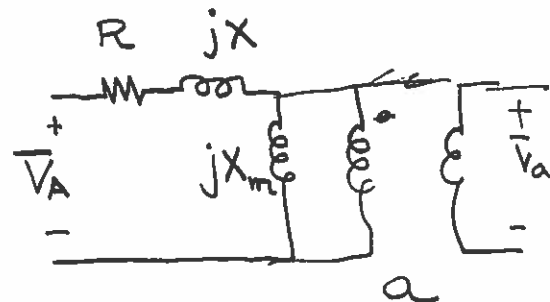


Δ - Δ TRANSFORMER

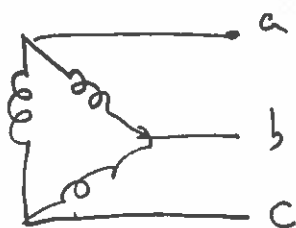
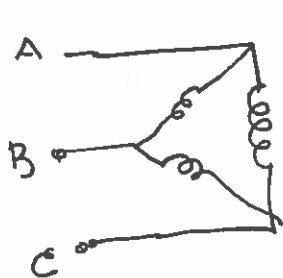
Similar to the Y-Y connection but all the parameter of the per-phase equivalent are divided by 3:


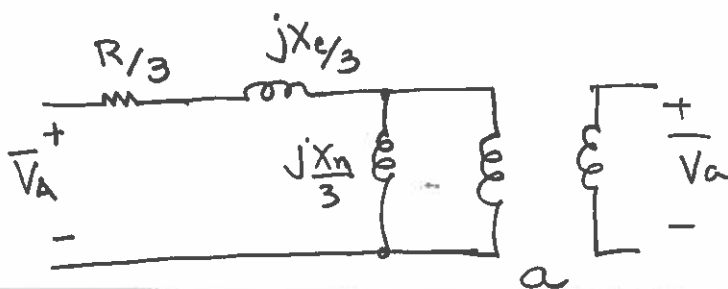
$$\frac{\bar{V}_{AB}}{\bar{V}_{ab}} = a \quad \frac{\bar{V}_{BC}}{\bar{V}_{bc}} = a \quad \frac{\bar{V}_{CA}}{\bar{V}_{ca}} = a$$



Δ -Y CONNECTION

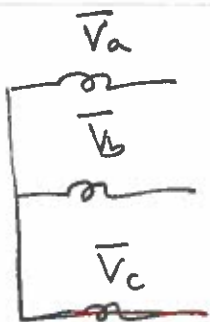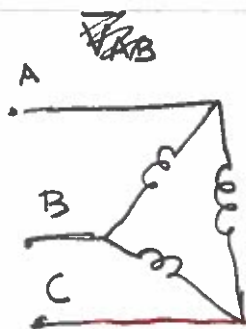

$$\frac{\bar{V}_{AB}}{\bar{V}_a} = a$$


$$\frac{\bar{V}_{BC}}{\bar{V}_b} = a$$

$$\frac{\bar{V}_{CA}}{\bar{V}_c} = a$$

$$\bar{V}_a = \frac{1}{\sqrt{3}} \bar{V}_{ab} e^{-j\pi/6}$$




$$\bar{V}_{AB} = a \cdot \frac{1}{\sqrt{3}} \bar{V}_{ab} e^{-j\pi/6} \rightarrow \bar{V}_{ab} = \frac{\sqrt{3}}{a} e^{+j\pi/6} \bar{V}_{AB}$$
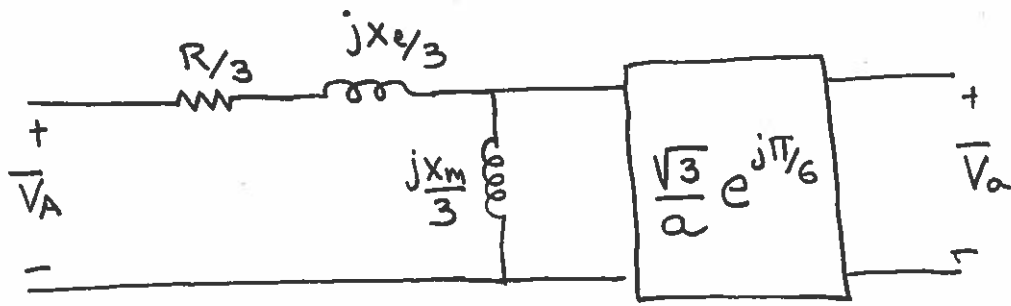
$$\bar{V}_a = \frac{\sqrt{3}}{a} e^{j\pi/6} \bar{V}_A$$



- Δ -Y CONNECTION introduces a 30° phase shift
- Common in distribution step-down since there is a neutral on the low voltage side.

Y- Δ CONNECTION

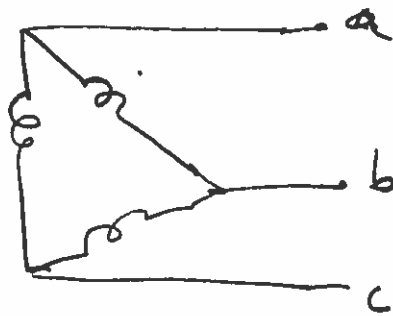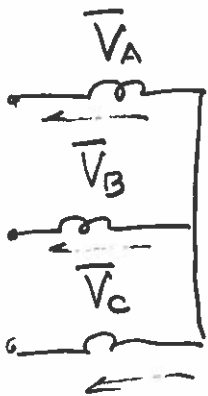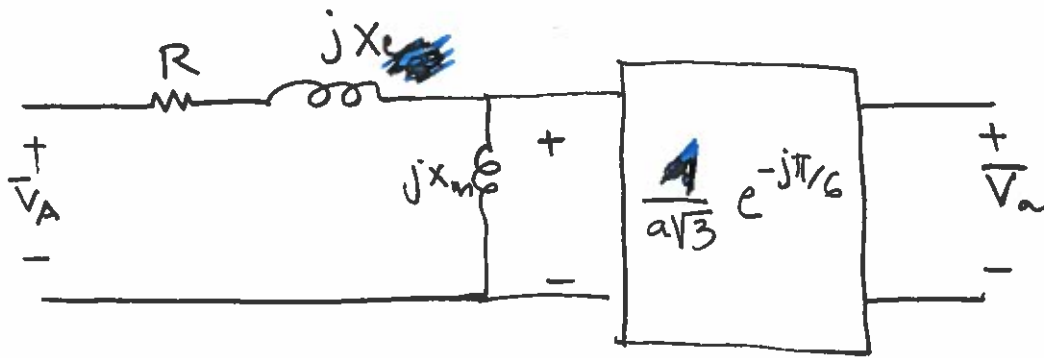

$$\bar{V}_A = a \bar{V}_{ab} = a\sqrt{3} e^{j\pi/6} \bar{V}_a$$

$$\bar{V}_A = a\sqrt{3} e^{j\pi/6} \bar{V}_a$$

$$\bar{V}_a = \frac{1}{a\sqrt{3}} e^{-j\pi/6} \bar{V}_A$$

$$\frac{\bar{V}_A}{\bar{V}_{ab}} = a \quad \bar{V}_A = \frac{1}{\sqrt{3}} \bar{V}_{AB} e^{-j\pi/6}$$

$$\frac{1}{\sqrt{3}} \bar{V}_{AB} e^{-j\pi/6} = a \bar{V}_{ab} \rightarrow \bar{V}_{ab} = \frac{1}{a\sqrt{3}} e^{-j\pi/6} \bar{V}_{AB}$$

$$\bar{V}_{AB} = \sqrt{3} a \bar{V}_{ab} e^{j\pi/6} \rightarrow \bar{V}_a = \frac{1}{\sqrt{3} \cdot a} e^{-j\pi/6} \bar{V}_A$$

