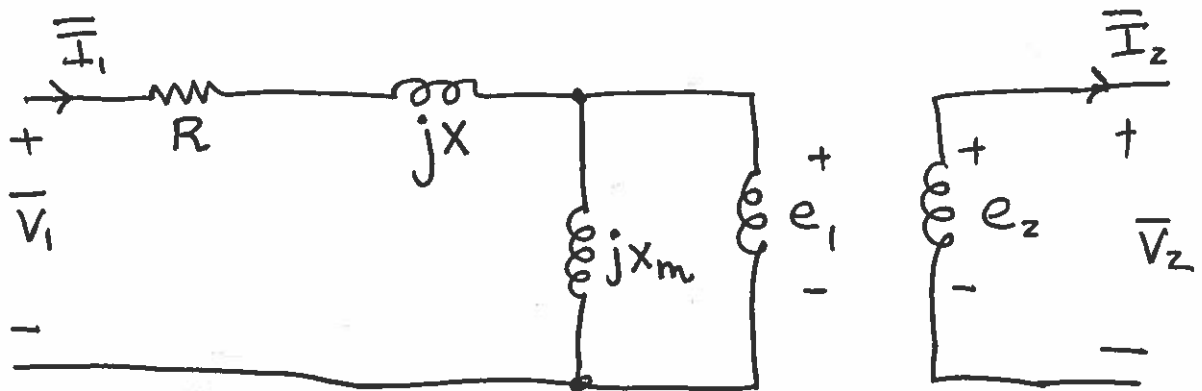


LECTURE 9

09/26/17


CALCULATION OF MODEL PARAMETERS



The parameters of the model can be determined based upon:

- (i) Nameplate data: Rated voltage and power
- (ii) Open-circuit test: rated voltage is applied to primary with secondary open; measure the primary current (and losses)
- (iii) Short-circuit test: with secondary shorted, apply voltage to primary to get rated current to flow; measure voltage and losses.


Example

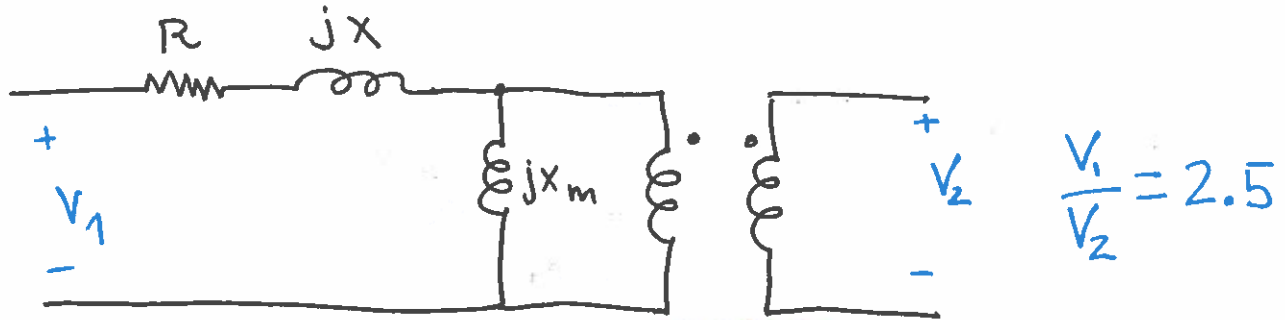

1 ϕ transformer: $S = 100\text{MVA}$, ~~200/80~~ $80/200$ KV

- Open-circuit test: 20A, 10KW losses
- Short-circuit test: 30KV, 500KW losses.

Short-circuit test

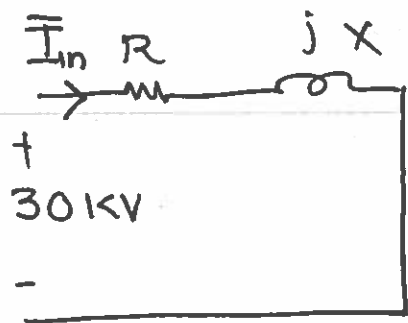

$$\bar{I}_{in} = \frac{100 \cdot 10^6}{80 \cdot 10^3} = 500\text{A}$$


$$\bar{Z} = R + jX \rightarrow Z = \frac{V}{I} = \frac{30 \cdot 10^3}{500} = 60 \Omega$$

$$P_{loss} = I^2 \cdot R = 500 \cdot 10^3$$

$$R = \frac{500 \cdot 10^3}{500^2} = \cancel{200} \Omega$$

$$Z = \sqrt{R^2 + X^2} \rightarrow X = \sqrt{60^2 - 2^2} \approx 60 \Omega$$

Open-circuit test

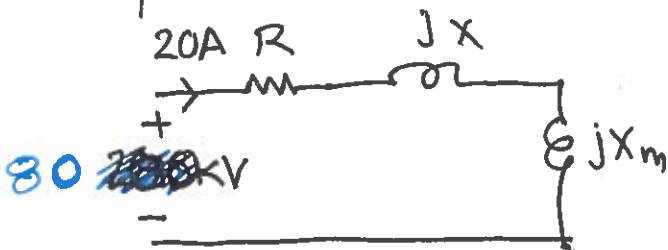

$$Z = R + j(X + X_m)$$

$$\frac{80 \cdot 10^3}{20} = Z = \cancel{4000} \Omega$$

$$= \sqrt{R^2 + (X + X_m)^2}$$

$$X_m \approx 10,000 \Omega$$

PER - UNIT NORMALIZATION

- In power system calculations, a normalization of variables called per-unit normalization is almost always used.
- As we will see, it is especially convenient if many transformers and voltages levels are involved.

- The idea is to pick base values for quantities such as
 - (i) Voltages
 - (ii) Currents
 - (iii) Impedances
 - (iv) Power
 - ...

and to define the quantity in per unit as follows:

$$\text{quantity in per unit} = \frac{\text{actual quantity}}{\text{base value quantity}}$$

- A vital point is that the base quantities are picked to satisfy the same kind of relationships as the actual variables.

- For example corresponding to $\bar{V} = \bar{Z} \cdot \bar{I}$ (actual variables in complex number)

we have the eqn. for base quantities

$$V_B = Z_B I_B$$


Dividing, we obtain

$$\bar{V}_{pu} = \bar{Z}_{pu} \bar{I}_{pu}$$


which has the same form as $\bar{V} = \bar{Z} \bar{I}$,
i.e., we can do circuit analysis with
the p.u. quantities.

Example

$$I = \frac{10}{1} = 10 \text{ A}$$

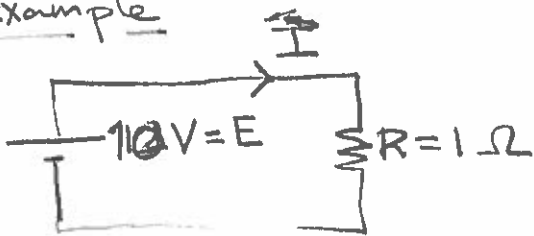

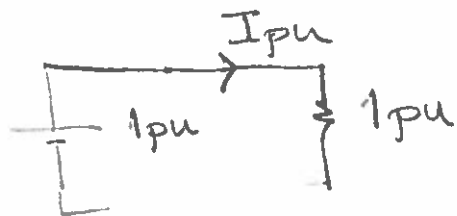
Pick: $V_B = 10 \text{ V}$, $\bar{Z}_B = 1 \Omega$, then $I_B = 10 \text{ A}$



$$I_{pu} = \frac{1}{1} = 1$$

$$I = I_B \times I_{pu} = 10 \text{ A}$$

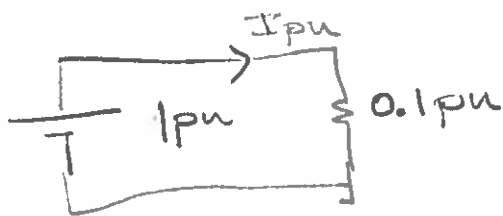Pick $V_B = 10$, $Z_B = 10 \Omega$, then $I_B = 1 \text{ A}$



$$I_{pu} = \frac{1}{0.1} = 10 \text{ pu}$$

$$I = I_B \times I_{pu} = 1 \text{ A} \times 10 = 10 \text{ A}$$

What we have done for Ohm's law,
can be done in the case of power
calculations

$$\bar{S} = \bar{V} \cdot \bar{I}^*$$

$$\Rightarrow \bar{S}_B = V_B I_B$$

$$\Rightarrow \bar{S}_{pu} = \bar{V}_{pu} \cdot \bar{I}_{pu}^*$$

where $\bar{S}_{pu} = \frac{\bar{S}}{S_B}$

$\bar{V}_{pu} = \frac{\bar{V}_1}{V_B}$

$\bar{I}_{pu} = \frac{\bar{I}}{I_B}$


Note that $\begin{cases} V_B = Z_B I_B \\ S_B = V_B I_B \end{cases}$ 4 variables, two eqns.

If we fix two base variables, the others are automatically determined.

• Pick S_B and V_B , then $\begin{cases} Z_B = \frac{V_B^2}{S_B} \\ I_B = \frac{S_B}{V_B} \end{cases}$ and $I_B = \frac{V_B}{Z_B}$

DEALING WITH TRANSFORMERS

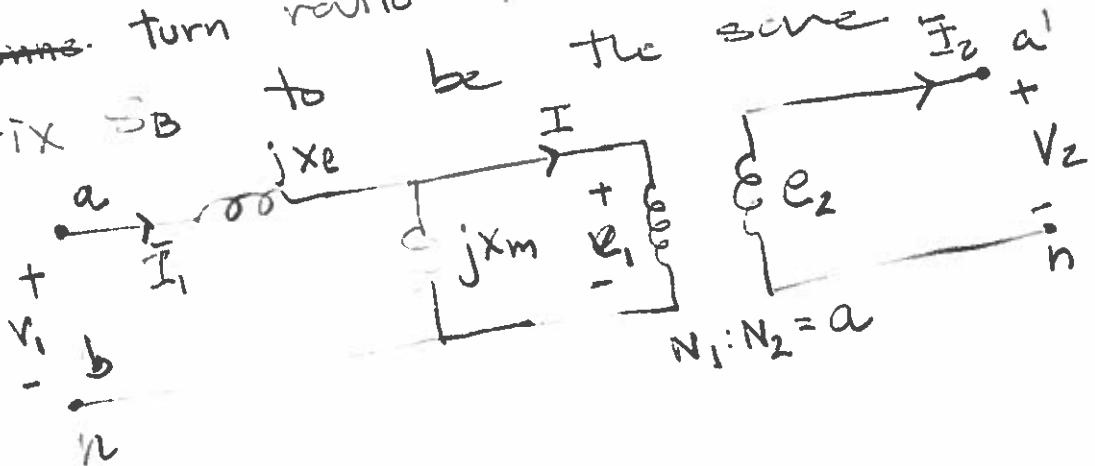- If the network includes transformers, there is an advantage to picking different bases for the two sides of the transformers.
- Suppose that we make the ratio of voltage bases equal to the ~~const.~~ turn ratio of the transformers.
- Fix S_B to be the same



$$S_B, V_{1B}, V_{2B} = \frac{1}{a} V_{1B}, I_{1B}, I_{2B} = a I_{1B},$$

$$Z_{2B} = \left(\frac{1}{a}\right)^2 Z_{1B}$$

$$\left\{ \begin{array}{l} V_{2pu} = \frac{V_2}{V_{2B}} = \frac{\frac{1}{a} e_1}{\frac{1}{a} V_{1B}} = e_{1pu} \\ I_{2pu} = \frac{I_2}{I_{2B}} = \frac{a I_1}{a I_{1B}} = I_{1pu} \end{array} \right.$$

→ We can redraw the circuit to show relations between per unit quantities but without the ideal transformer!

