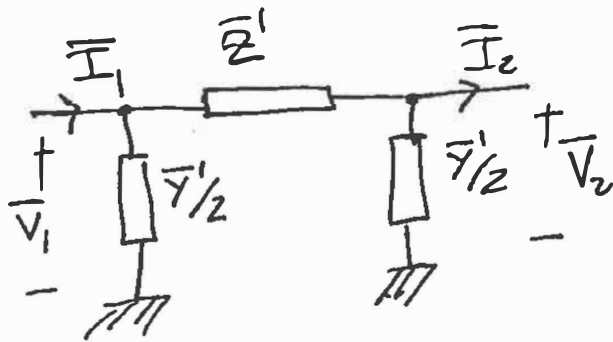


## LECTURE 7

09/19/17

## LUMPED-PARAMETER CIRCUIT MODEL (TT MODEL)



$$\bar{V}_1 = \bar{V}_2 + \bar{Z}'(\bar{I}_2 + \frac{\bar{Y}'}{2}\bar{V}_2)$$

$$= (1 + \bar{Z}' \cdot \frac{\bar{Y}'}{2})\bar{V}_2 + \bar{Z}' \cdot \bar{I}_2$$

$$\bar{Z}' = \bar{Z}_c \cdot \sinh \gamma d$$

$$\bar{Z}' = \sqrt{\frac{\bar{Z}}{\bar{Y}}} \cdot \frac{\gamma d}{\gamma d} \sinh \gamma d$$

$$= \sqrt{\frac{\bar{Z}}{\bar{Y}}} \cdot \sqrt{\bar{Z} \cdot \bar{Y}} \cdot d \cdot \frac{\sinh \gamma d}{\gamma d}$$

$$= \underbrace{\bar{Z} \cdot d}_{\bar{Z}_1} \cdot \frac{\sinh \gamma d}{\gamma d}$$

$$\bar{Z}' = \bar{Z}_1 \cdot \frac{\sinh \gamma d}{\gamma d}, \quad \bar{Z}_1 = \bar{Z} \cdot d$$

$$1 + \bar{Z}' \cdot \frac{\bar{Y}'}{2} = \cosh \gamma d$$

$$\frac{\bar{Y}'}{2} = \frac{1}{\bar{Z}'} (\cosh \gamma d - 1) = \frac{1}{\bar{Z}_c} \frac{\cosh \gamma d - 1}{\sinh \gamma d}$$

$$= \frac{1}{\bar{Z}_c} \tanh \frac{\gamma d}{2} = \frac{\gamma d/2}{\bar{Z}_c} \frac{\tanh \frac{\gamma d}{2}}{\frac{\gamma d}{2}}$$

$$= \frac{\sqrt{\bar{Z} \bar{Y}} d/2}{\sqrt{\bar{Z}/\bar{Y}}} \frac{\tanh \frac{\gamma d}{2}}{\frac{\gamma d}{2}} = \frac{\bar{Y} d}{2} \frac{\tanh \frac{\gamma d}{2}}{\frac{\gamma d}{2}}$$

$$\bar{Z}' = \bar{Z} \cdot \frac{\sinh \gamma d}{\gamma d}$$

$$\frac{\bar{Y}'}{2} = \frac{\bar{Y}}{2} \frac{\tanh \gamma d/2}{\gamma d/2}$$

$$\bar{Z} = \bar{Z} \cdot d$$

$$\frac{\bar{Y}}{2} = \bar{Y}/2$$

### SIMPLIFIED MODELS

length d	$\bar{Z}'$	$\bar{Y}'/2$
$d > 200$ miles	$\bar{Z} \frac{\sinh \gamma d}{\gamma d}$	$\frac{\bar{Y}}{2} \frac{\tanh \gamma d/2}{\gamma d/2}$
$50 \text{ miles} < d < 200 \text{ miles}$	$\bar{Z}$	$\bar{Y}/2$
$d < 50$ miles	$\bar{Z}$	0


### LOSSLESS TRANSMISSION LINE

- $r = 0$

- $\bar{Z}_c = \sqrt{j\omega L \frac{1}{j\omega C}} = \sqrt{\frac{L}{C}} = \sqrt{\frac{L}{C}} \text{ } [\Omega]$

- The characteristic impedance in this case is referred to as the SURGE IMPEDANCE

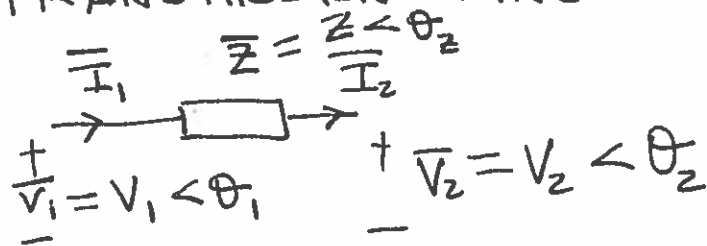POWER TRANSFER THROUGH A SHORT TRANSMISSION LINE



$$\bar{S}_{12} = \bar{V}_1 \cdot \bar{I}_1^* = \bar{V}_1 \cdot \frac{(\bar{V}_1 - \bar{V}_2)^*}{\bar{Z}^*}$$

$$\bar{V}_1 = V_1 \angle \theta_1, \quad \bar{V}_2 = V_2 \angle \theta_2, \quad \bar{Z} = Z \angle \theta_2$$

$$\bar{S}_{12} = V_1 \angle \theta_1 \frac{V_1 \angle -\theta_1 - V_2 \angle -\theta_2}{Z \angle -\theta_2}$$

$$= \frac{V_1^2}{Z} \angle \theta_2 - \frac{V_1 V_2}{Z} \angle \theta_1 - \theta_2 + \theta_2$$

If the line is lossless  $\theta_2 = \frac{\pi}{2}$

$$\bar{S}_{12} = \frac{V_1^2}{Z} \angle \frac{\pi}{2} - \frac{V_1 V_2}{Z} \angle \theta_1 - \theta_2 + \frac{\pi}{2}$$

$$P_{12} = \text{Re} \{ \bar{S}_{12} \} = - \frac{V_1 V_2}{Z} \cos \left( \theta_1 - \theta_2 + \frac{\pi}{2} \right)$$

$$= \frac{V_1 V_2}{Z} \sin (\theta_1 - \theta_2)$$

$$Q_{12} = \text{Im} \{ \bar{S}_{12} \} = \frac{V_1^2}{Z} - \frac{V_1 V_2}{Z} \sin \left( \theta_1 - \theta_2 + \frac{\pi}{2} \right)$$

$$= \frac{V_1^2}{Z} - \frac{V_1 V_2}{Z} \cos (\theta_1 - \theta_2)$$


# TRANSFORMERS

## - THE NEED FOR TRANSFORMERS

- (i) The generation of electric power is usually done at voltages that range between 11 and 13 kV
- (ii) Efficient power transmission over long distances requires much higher voltages than those at which power is generated. Typically values used in power transmission are 138, 230, 345, 765 kV
- (iii) Distribution of power to our neighborhood and industrial plants is done at much lower voltages: 2400-4600V
- (iv) In our houses, the voltage is 240/120V

In view of (i)-(iv), we need a way to step voltages up and down. The device that permits AC voltages to be stepped UP & DOWN is the transformer. [DC voltage can also be stepped up and down using power electronics → ECE 464/469.]


# 1-∅ IDEAL TRANSFORMER MODEL

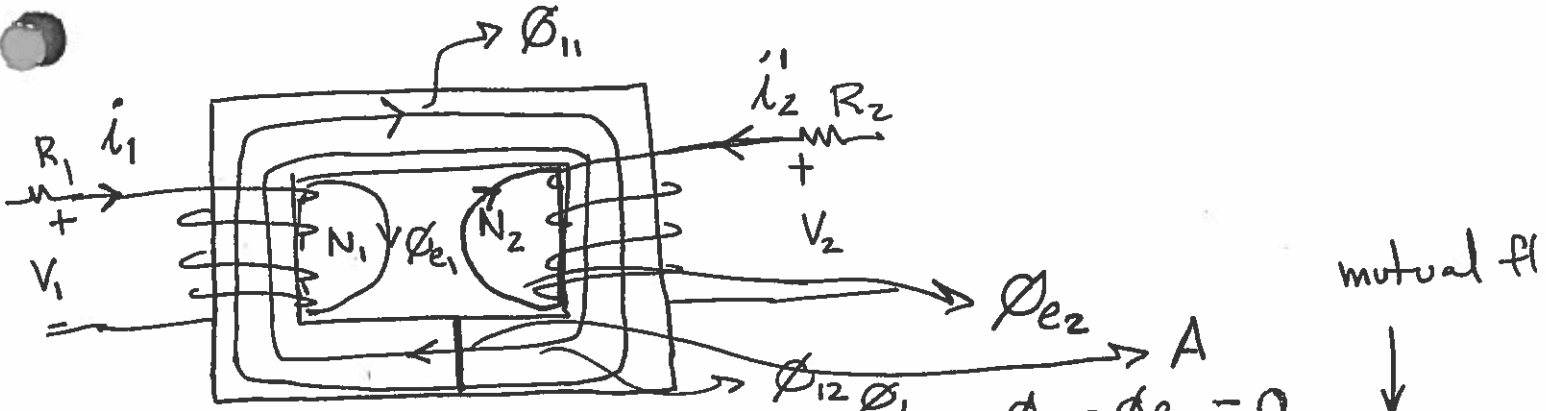

$$\left\{ \begin{array}{l} \lambda_1 = N_1 \cdot \Phi_1 = N_1 (\Phi_{11} + \Phi_{12} + \Phi_{e1}) \\ \lambda_2 = N_2 \cdot \Phi_2 = N_2 (\Phi_{22} + \Phi_{21} + \Phi_{e2}) \end{array} \right\} \begin{array}{l} \Phi_{e1} = \Phi_{e2} = 0 \\ \rightarrow \Phi_1 = \Phi_2 = \Phi_m \end{array}$$

$$\left\{ \begin{array}{l} V_1 = \frac{d\lambda_1}{dt} + R_1 \dot{i}_1 \\ V_2 = \frac{d\lambda_2}{dt} + R_2 \dot{i}_2 \end{array} \right\} \begin{array}{l} R_1 = R_2 = 0 \\ V_1 = \frac{d\lambda_1}{dt} = N_1 \frac{d\Phi_m}{dt} \\ V_2 = \frac{d\lambda_2}{dt} = N_2 \frac{d\Phi_m}{dt} \end{array} \rightarrow \boxed{\frac{V_1}{V_2} = \frac{N_1}{N_2}}$$

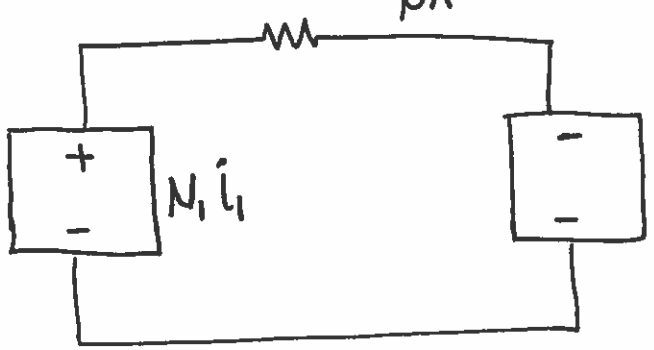- Assumptions for an ideal transformer:
- No losses :  $R_1 = R_2 = 0$  (also no magnetic losses)
  - No leakage fluxes :  $\Phi_{e1} = \Phi_{e2}$
  - Magnetic core material has infinite permeability,



$$\mu \rightarrow \infty \rightarrow R \rightarrow 0$$


$$N_1 \dot{i}_1 + N_2 \dot{i}_2 = 0$$

$$\boxed{\frac{\dot{i}_1}{\dot{i}_2} = -\frac{N_2}{N_1}}$$

The two fundamental relations for a single-phase transformer are:

$$\frac{V_1}{V_2} = \frac{N_1}{N_2}$$

$$\frac{i_1}{i_2'} = - \frac{N_2}{N_1}$$

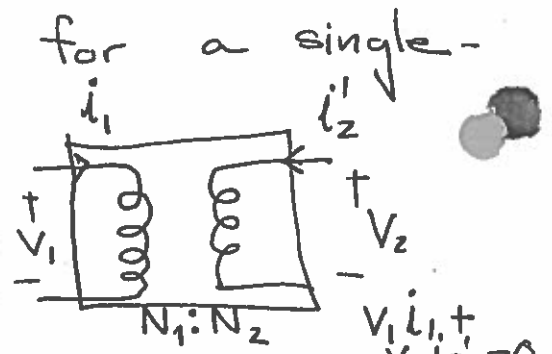


We can reverse the current on the "2" side:

$$i_2 := -i_2'$$

$$\frac{V_1}{V_2} = \frac{N_1}{N_2}$$


$$\frac{i_1}{i_2} = \frac{N_1}{N_2}$$

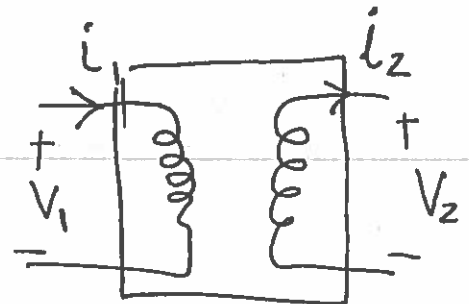

$$\underbrace{V_1 i_1}_{\text{Power in}} = \underbrace{V_2 i_2}_{\text{Power out}}$$

Turn ratio:  $a := \frac{N_1}{N_2}$

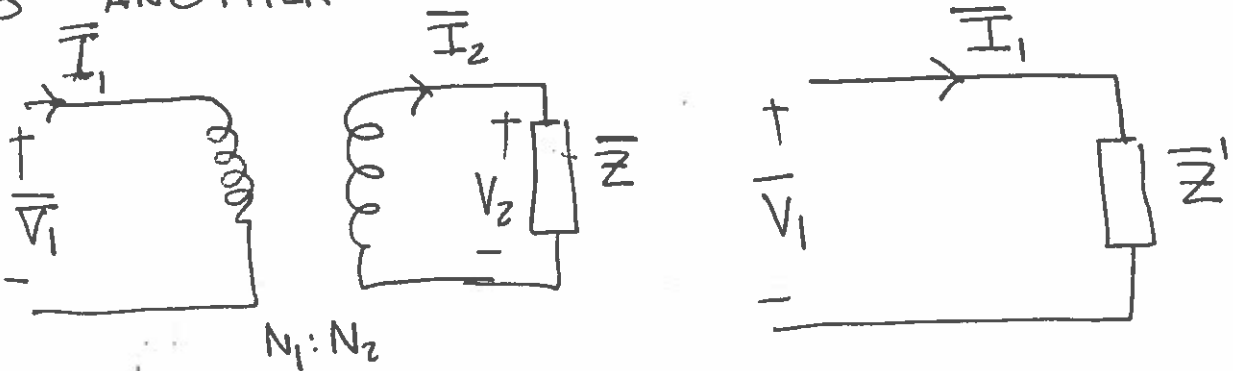REFERRING AN IMPEDANCE FROM ONE SIDE TO ANOTHER



$$\bar{V}_2 = \bar{I}_2 \cdot \bar{Z}$$

$$\frac{\bar{V}_1}{\bar{V}_2} = \frac{N_1}{N_2} \rightarrow \bar{V}_2 = \frac{N_2}{N_1} \bar{V}_1$$

T

$$\frac{\bar{I}_1}{\bar{I}_2} = \frac{N_2}{N_1} \rightarrow \bar{I}_2 = \frac{N_1}{N_2} \bar{I}_1$$

$$\frac{N_2}{N_1} \bar{V}_1 = \frac{N_1}{N_2} \bar{I}_1 \cdot \bar{Z} \rightarrow \bar{V}_1 = \bar{I}_1 \left( \frac{N_1}{N_2} \right)^2 \bar{Z}$$

$$\bar{Z}' = \left( \frac{N_1}{N_2} \right)^2 \bar{Z}$$