

11/30/17


LECTURE 23

UNBALANCED SYSTEM OPERATION

- COMMON TYPES OF FAULTS
- METHOD OF SYMMETRICAL COMPONENTS
- USE OF SYMMETRICAL COMPONENTS FOR FAULT ANALYSIS


UNBALANCED SYSTEM OPERATION

- So far, we have assumed that the power system works in a balanced condition (this goes back to the very beginning of the course)
- This is the case in the absence of faults.
- When the system operates in a balanced condition, we saw that the analysis simplifies to look at just one phase using per-phase equivalents.
- Balance operation is no longer true when a fault occurs. (except for 3ϕ faults which are rare).

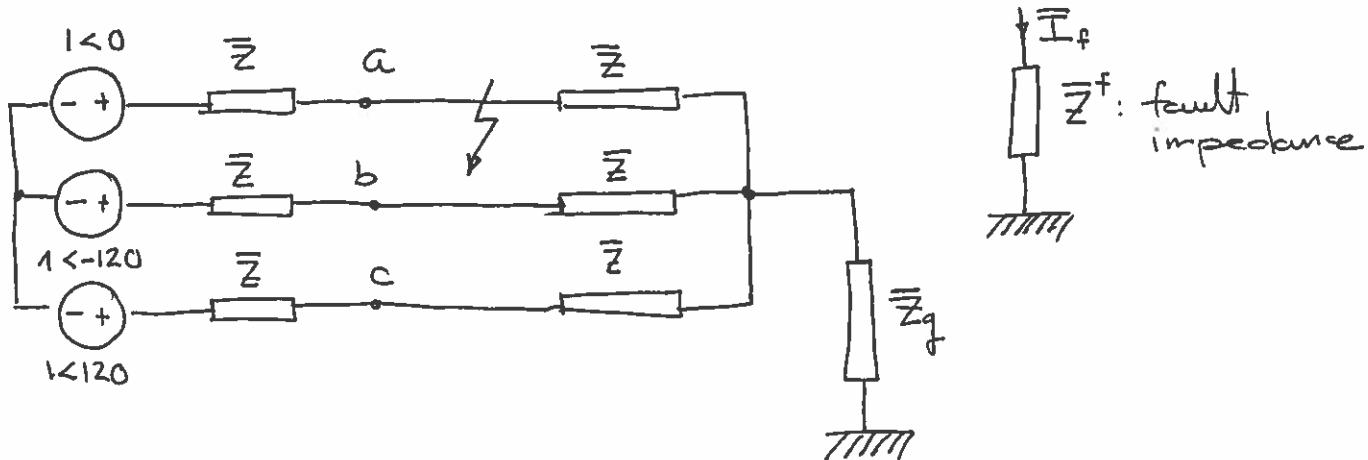

- We need analysis techniques to compute fault currents and other electrical variables.
- These techniques are then used to select appropriate circuit breaker ratings for example.

COMMON TYPES OF FAULTS

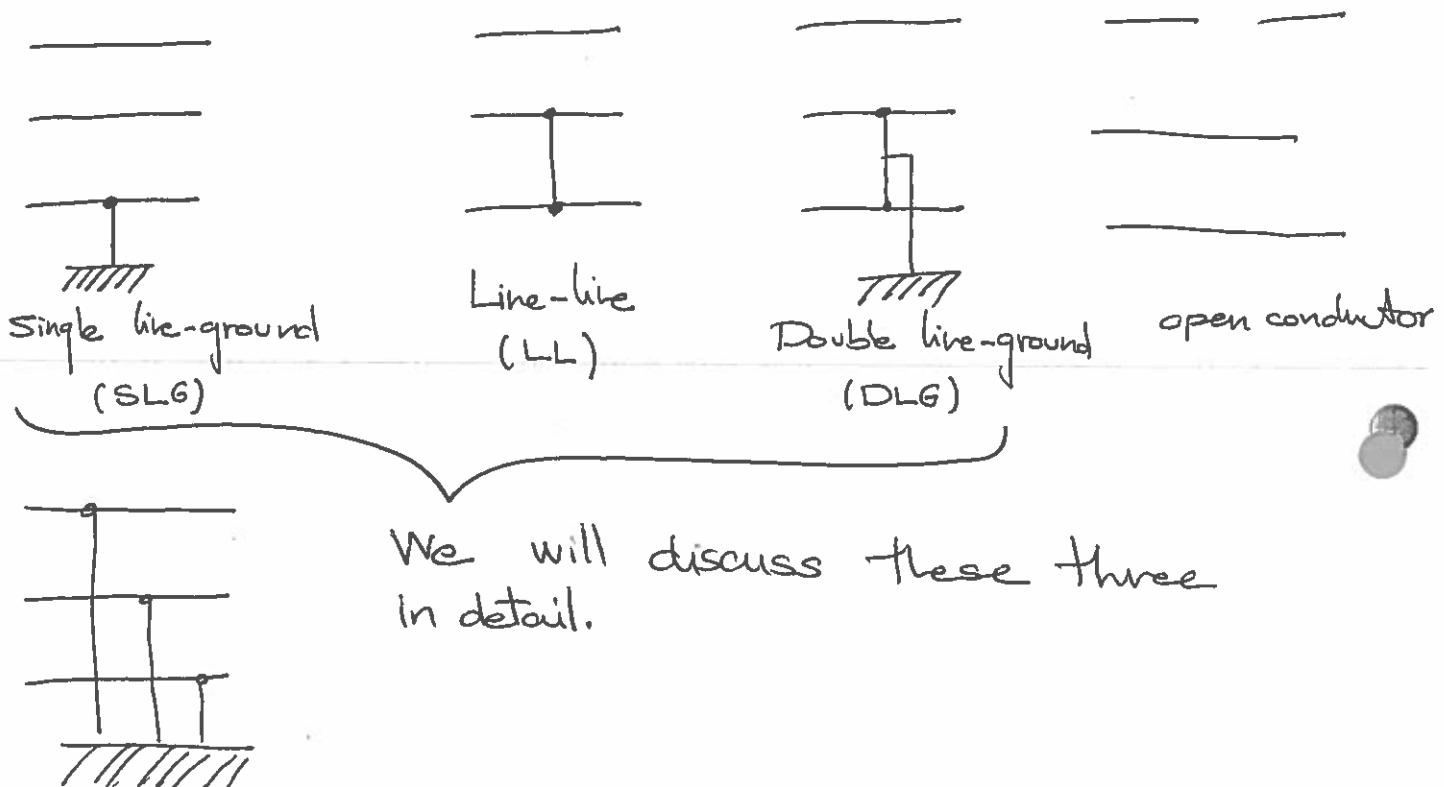


We will discuss these three in detail.

Balanced three-phase-ground -

METHOD OF SYMMETRICAL COMPONENTS

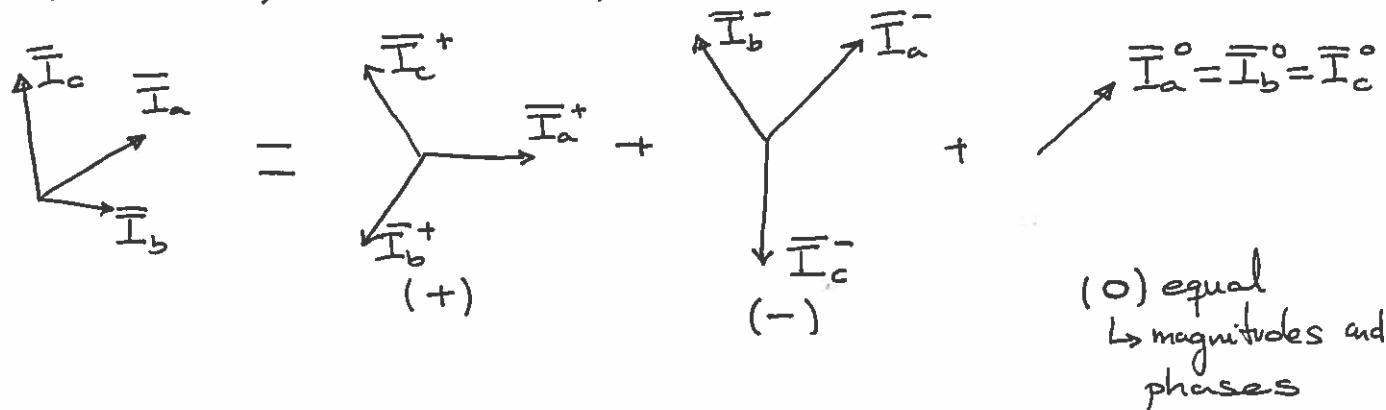- Due to Fortesque, it is the main engine to analyze unbalanced power systems.
- The method of symmetrical components allows to represent any set of three phasor, say \bar{I}_a , \bar{I}_b , \bar{I}_c in terms of nine symmetrical components:
 $\bar{I}_a^0, \bar{I}_a^+, \bar{I}_a^-, \bar{I}_b^0, \bar{I}_b^+, \bar{I}_b^-, \bar{I}_c^0, \bar{I}_c^+, \bar{I}_c^-$



In matrix form

$$\begin{bmatrix} \bar{I}_a \\ \bar{I}_b \\ \bar{I}_c \end{bmatrix} = \begin{bmatrix} \bar{I}_a^0 \\ \bar{I}_b^0 \\ \bar{I}_c^0 \end{bmatrix} + \begin{bmatrix} \bar{I}_a^+ \\ \bar{I}_b^+ \\ \bar{I}_c^+ \end{bmatrix} + \begin{bmatrix} \bar{I}_a^- \\ \bar{I}_b^- \\ \bar{I}_c^- \end{bmatrix}$$

Define $\alpha = 1 < 120^\circ$

As we know

$$\begin{aligned} \bar{I}_b^+ &= \alpha^2 \bar{I}_a^+ & \bar{I}_c^+ &= \alpha \bar{I}_a^+ \\ \bar{I}_b^- &= \alpha \bar{I}_b^- & \bar{I}_c^- &= \alpha^2 \bar{I}_c^- \end{aligned}$$

$$\begin{bmatrix} \bar{I}_a \\ \bar{I}_b \\ \bar{I}_c \end{bmatrix} = \underbrace{\begin{bmatrix} 1 & 1 & 1 \\ 1 & \alpha^2 & \alpha \\ 1 & \alpha & \alpha^2 \end{bmatrix}}_{\bar{A}} \begin{bmatrix} \bar{I}_a^0 \\ \bar{I}_a^+ \\ \bar{I}_a^- \end{bmatrix}$$

$$\bar{I} \triangleq \begin{bmatrix} \bar{I}_a \\ \bar{I}_b \\ \bar{I}_c \end{bmatrix}$$

$$\bar{I}_s \triangleq \begin{bmatrix} \bar{I}_a^0 \\ \bar{I}_b^0 \\ \bar{I}_c^0 \end{bmatrix}$$


If we know $\bar{I}_a, \bar{I}_b, \bar{I}_c$, it is easy to find the symmetrical components as follows

$$\bar{I} = \bar{A} \cdot \bar{I}_s \rightarrow \bar{I}_s = \bar{A}^{-1} \cdot \bar{I} \quad \text{where}$$

$$\bar{A}^{-1} = \frac{1}{3} \begin{bmatrix} 1 & 1 & 1 \\ 1 & \alpha & \alpha^2 \\ 1 & \alpha^2 & \alpha \end{bmatrix}$$

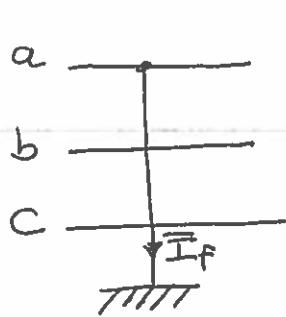Example : finding symmetrical components of SLG currents


→ Suppose we are given the fault current. If in phase of a three-phase system



$$\bar{I} = \begin{bmatrix} \bar{I}_f \\ 0 \\ 0 \end{bmatrix}$$

$$\begin{bmatrix} \bar{I}_a^0 \\ \bar{I}_a^+ \\ \bar{I}_a^- \end{bmatrix} = \frac{1}{3} \begin{bmatrix} 1 & 1 & 1 \\ 1 & \alpha & \alpha^2 \\ 1 & \alpha^2 & \alpha \end{bmatrix} \begin{bmatrix} \bar{I}_f \\ 0 \\ 0 \end{bmatrix}$$

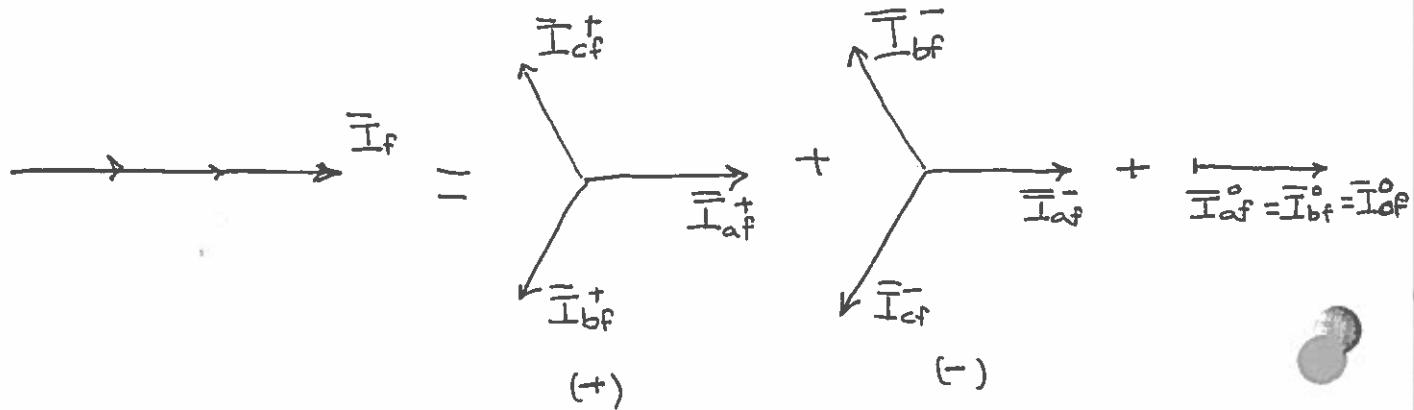
$$\begin{bmatrix} \bar{I}_a^0 \\ \bar{I}_a^+ \\ \bar{I}_a^- \end{bmatrix} = \bar{I}_f \begin{bmatrix} 1 \\ 1 \\ 1 \end{bmatrix} \rightarrow \bar{I}_a^0 = \bar{I}_a^+ = \bar{I}_a^- = \frac{1}{3} \bar{I}_f$$




USE OF SYMMETRICAL COMPONENTS FOR FAULT ANALYSIS

To introduce the method of symmetrical components for finding voltages and currents


LINE-GROUND FAULT

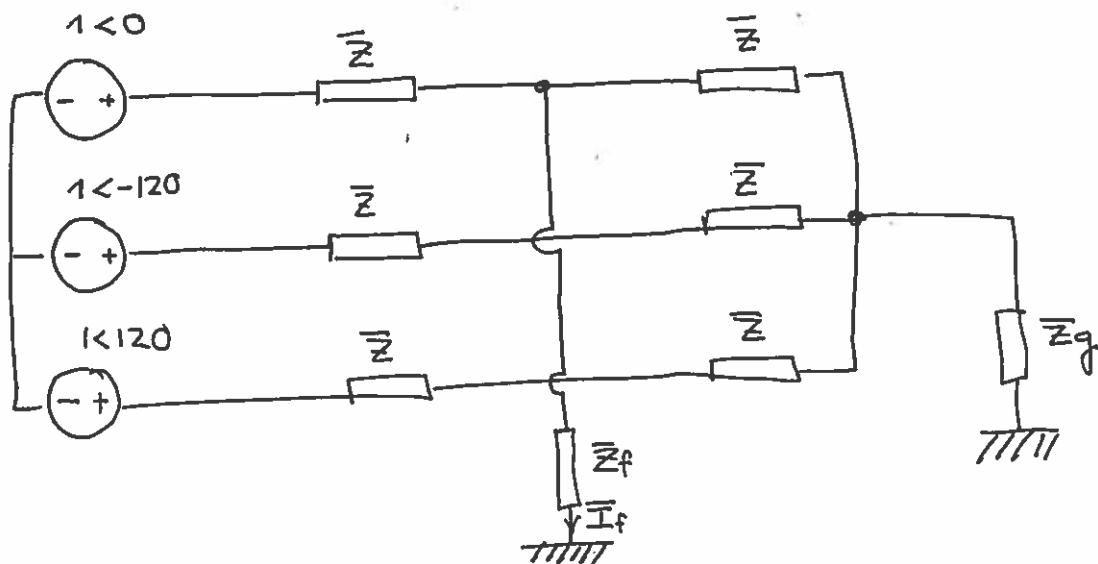

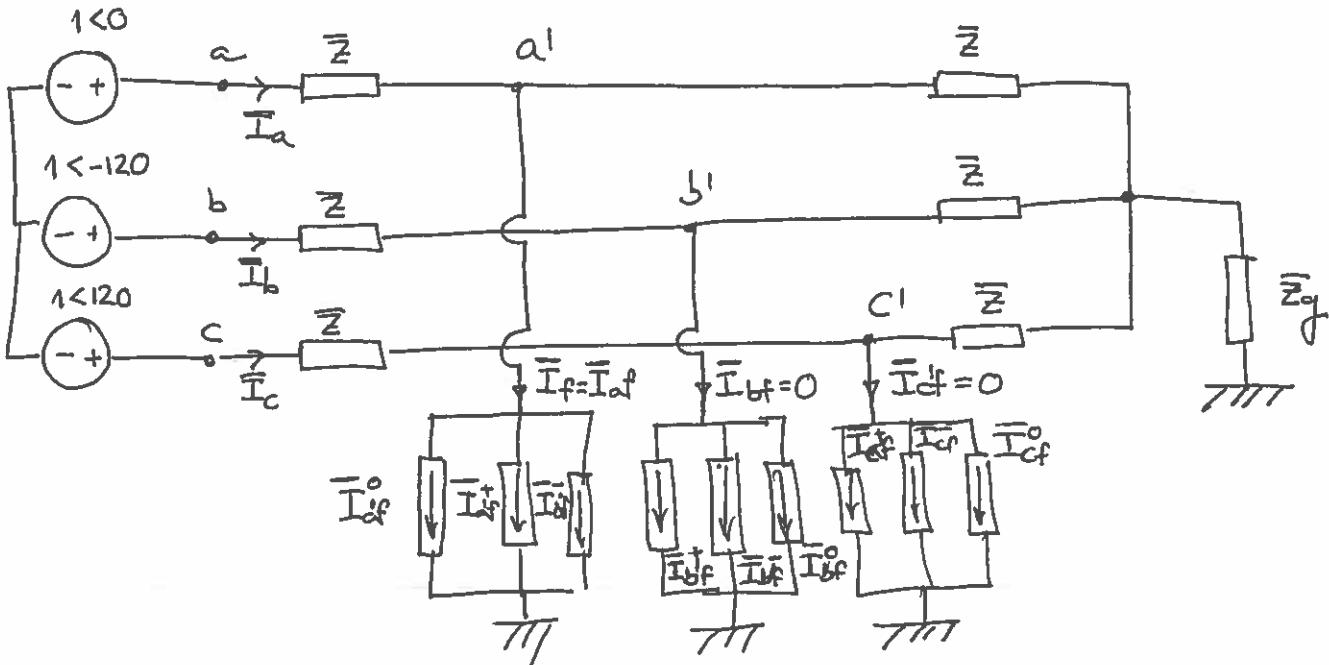- It is obvious that we cannot use per-phase equivalents as the circuit is not symmetric.
- Let's replace the impedance by a current source of the same magnitude as \bar{I}_f and write the current through each phase of the fault using symmetrical components.



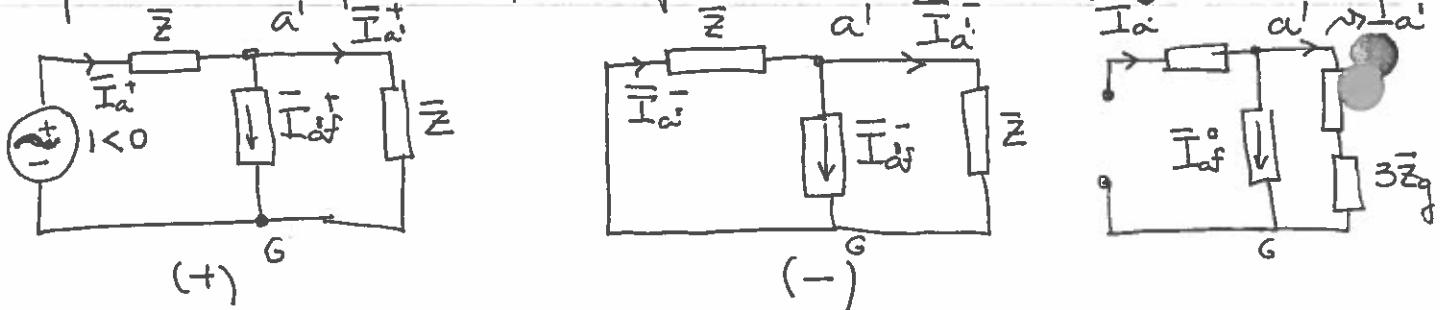We can apply superposition and solve each sequence independently using per-phase equivalents



- The voltage source of the (+) sequence is obvious
- The sc in the (-) replacing the voltage source is also intuitive (this is how we do it in superposition)
- The oc in the (0) is not so intuitive:

$\bar{I}_a^0 = \bar{I}_b^0 = \bar{I}_c^0$, but since the neutral (on the source) is isolated $\bar{I}_a^0 + \bar{I}_b^0 + \bar{I}_c^0 = 0 \Rightarrow$

$$\Rightarrow \bar{I}_a^0 = \bar{I}_b^0 = \bar{I}_c^0 = 0$$

$$\bar{I}_{a'}^0 = \bar{I}_{b'}^0 = \bar{I}_{c'}^0 : \bar{V}_{a'g}^0 = \bar{Z} \bar{I}_{a'}^0 + 3\bar{Z}_g \bar{I}_{a'}^0$$

SEQUENCE NETWORK CONNECTIONS FOR LINE-GROUND FAULT

The use of symmetrical components is even more appealing if we make the following observation

$$\left\{ \begin{array}{l} \bar{V}_{a'g} = \bar{V}_{a'g}^+ + \bar{V}_{a'g}^- + \bar{V}_{a'g}^0 \quad (\text{from superposition}) \\ \bar{I}_{af}^+ = \bar{I}_{af}^- = \bar{I}_{af}^0 = \frac{\bar{I}_f}{3} \end{array} \right.$$

$$\text{Also: } \bar{V}_{a'g} = \bar{Z}_f \cdot \bar{I}_f = 3 \cdot \bar{Z}_f \cdot \frac{\bar{I}_f}{3}$$

This two equations suggest that we can place the three sequence networks in series:

