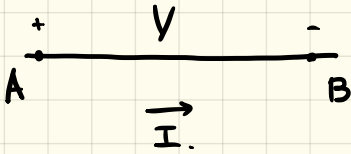


## Lecture 3:

① Wires:



$$\underline{V=0 \text{ for any } I.}$$


Two points in a circuit connected by a wire are said to be shorted together.

② Resistor: An element that has resistance.

Resistance: Voltage required to push current through an element.

Units: Ohm ( $\Omega$ )



$$1\Omega = \frac{1V}{1A}$$

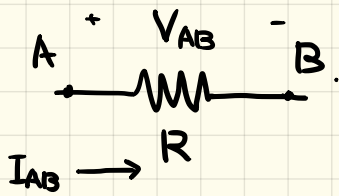

$$V_{AB} = V_A - V_B.$$

Ohm's law captures the relationship between the voltage across a resistor and the current through it.



$$V_{AB} = I_{AB} \cdot R.$$

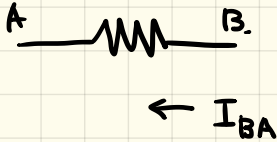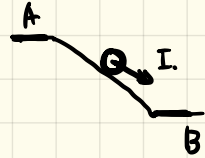

$$V_{BA} = I_{BA} \cdot R.$$

$$V_{AB} = -I_{BA} \cdot R = -V_{BA}.$$

# Example!

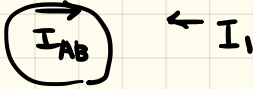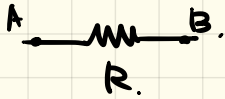

$$① \quad V_{AB} = 10V. \quad R = 1.$$

$$I_{AB} = ?$$

$$V_{AB} = I_{AB} \cdot R. \quad I_{AB} = 10.$$

$$② \quad \underline{V_{AB} = -10V} \quad R = 1.$$

$$I_{AB} = ?$$

$$V_{AB} = I_{AB} \cdot R. \quad I_{AB} = \underline{-10}.$$



$$③ \quad \left. \begin{array}{l} I_1 = -1A. \\ R = 1. \end{array} \right\} \underline{V_{AB} = ?} = 1V$$

$$I_1 = \underline{I_{BA}}$$

$$V_{BA} = I_{BA} \cdot R. = -1V.$$

Note:


① Low R:  $I = \frac{V}{R}$        $R \downarrow \rightarrow I \uparrow$ .

Large R:                       $R \uparrow \rightarrow I \downarrow$


② I-V curve.

$$I = \left(\frac{1}{R}\right) \cdot V$$

$$y = a \cdot x.$$

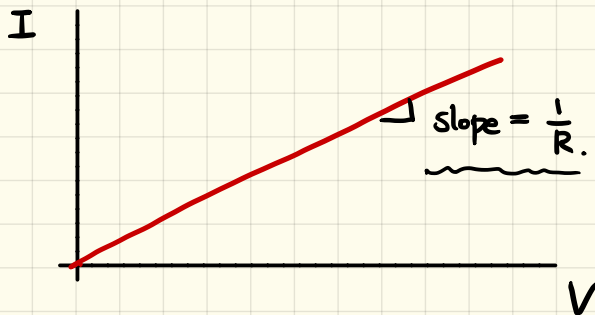


Example:

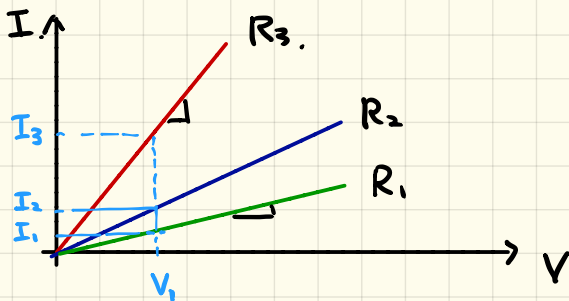

Rank resistors:

$$R_1 > R_2 > \underline{R_3}.$$


Example:

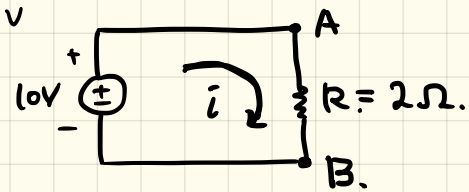

$$\bar{i} = I_{AB}$$

$$V_{AB} = \bar{i} \cdot R.$$

$$\bar{i} = 10/2 = 5A.$$

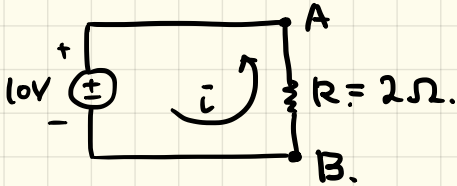


$$\bar{i} = -5A.$$

$$\bar{i} = I_{BA}$$

$$V_{BA} = \bar{i} \cdot R.$$

$$\bar{i} = -10/2 = -5A.$$

Power

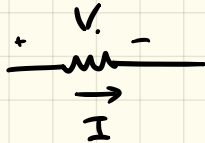

$$P = V \cdot I$$

$$V = IR.$$



$$P = IR \cdot I = \underline{I^2 R} > 0 \quad R > 0.$$

$$\text{or} = V \cdot \frac{V}{R} = \frac{V^2}{R} > 0$$


$\Rightarrow$  Resistor is a passive element :  $P > 0$ .
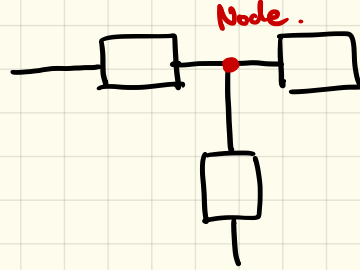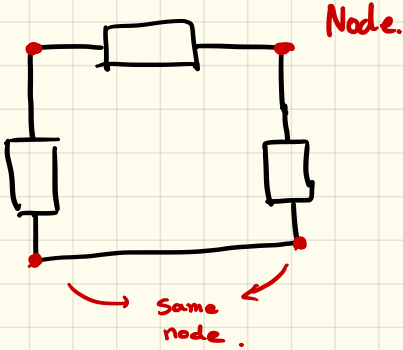
# Circuit Analysis.

Node : Point at which two or more elements are connected.



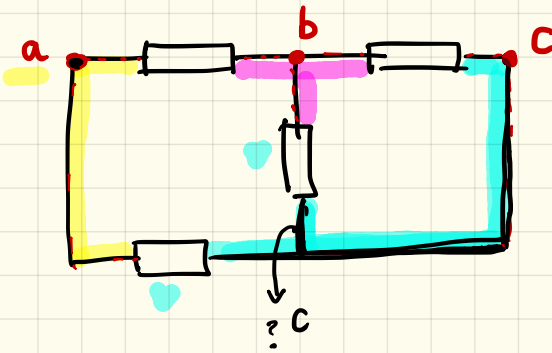note: Points connected by wires = same node.




3 independent nodes.
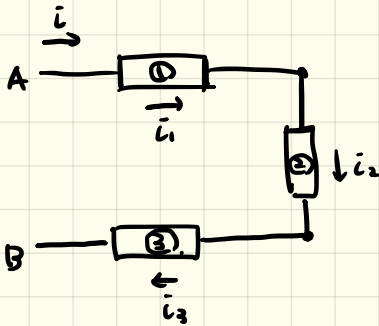
## Series connected elements :

Elements are said to be in series if

- ① They share one common node.
- ② The elements carry the same current.



①, ②, ③. carry same current.

$$i_1 = i_2 = i_3 = i.$$

## Series Resistors :




In general ,


$$R_{eq} = \sum_{k=1}^N R_k$$
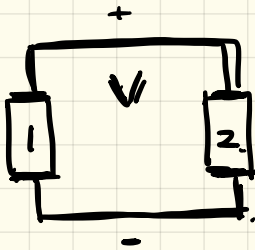
# Parallel elements.

Two elements in parallel if both ends of one element are connected to both ends of another one



Note:

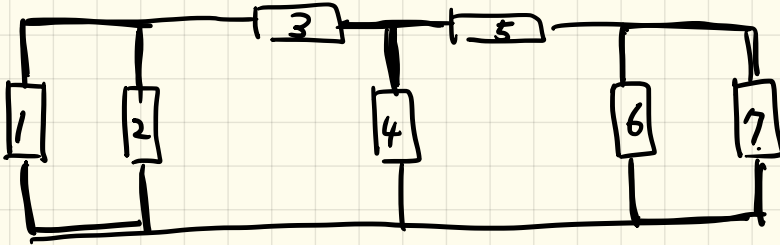

parallel connection?


6-7, 1-2.

series " ?

No.



Resistors in parallel.

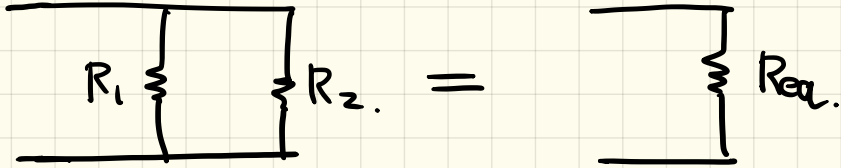

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}.$$

$$\Rightarrow R_{eq} = \frac{R_1 R_2}{R_1 + R_2}.$$

In general,

$$\frac{1}{R_{eq}} = \sum_{k=1}^N \frac{1}{R_k}$$

denoted by

$$R_{eq} = R_1 // R_2 // \dots // R_N.$$